

Date:

## EXPERIMENT NO. 4


**AIM:** Implement arithmetic and logic unit circuits in Logisim.

**OBJECTIVES:**


- i. Implement 1-bit, 2-bit, 4-bit and 8-bit arithmetic unit circuits
- ii. Implement 1-bit, 2-bit, 4-bit and 8-bit logical unit circuits for four logical functions
- iii. Implement 1-bit and 2-bit logical unit circuits for sixteen logical functions
- iv. Implement 2-bit, 4-bit and 8-bit bidirectional shifter
- v. Implement 1-bit, 2-bit, 4-bit and 8-bit ALU

**CIRCUITS:**


**i. 1) 1-bit arithmetic**

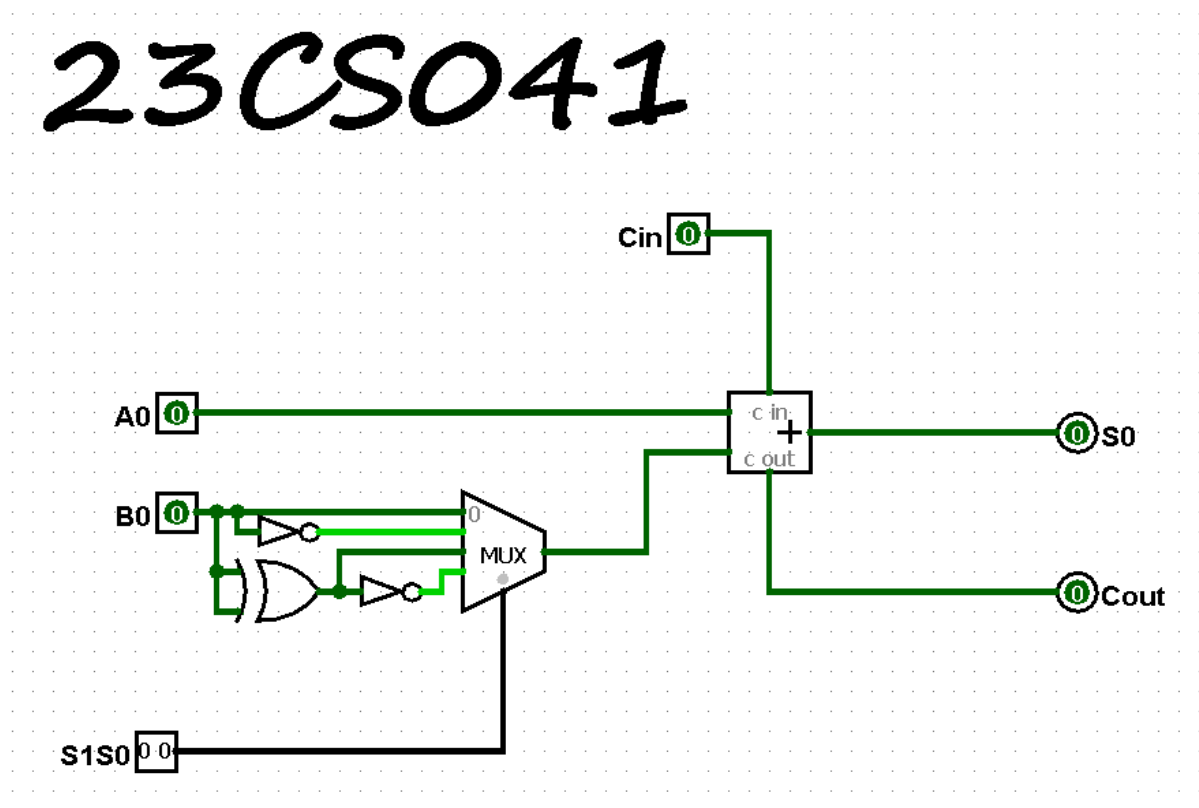


## 2) 2-bit arithmetic

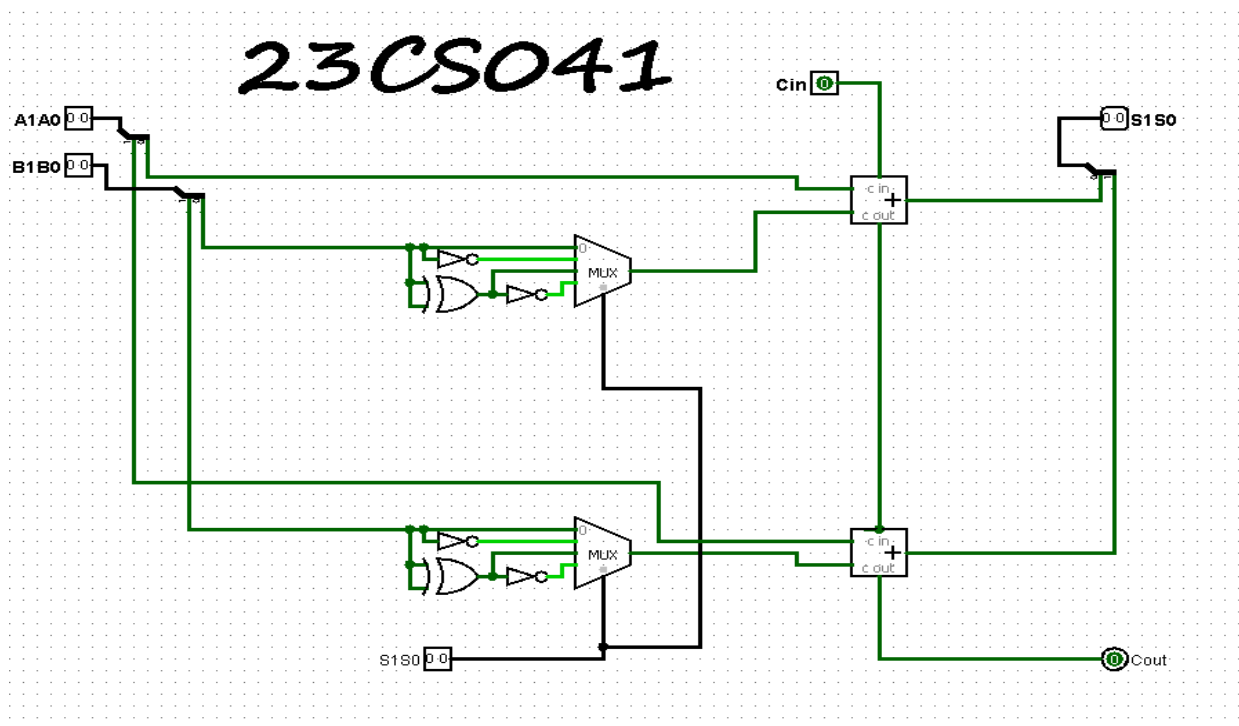


## 3) 4-bit arithmetic

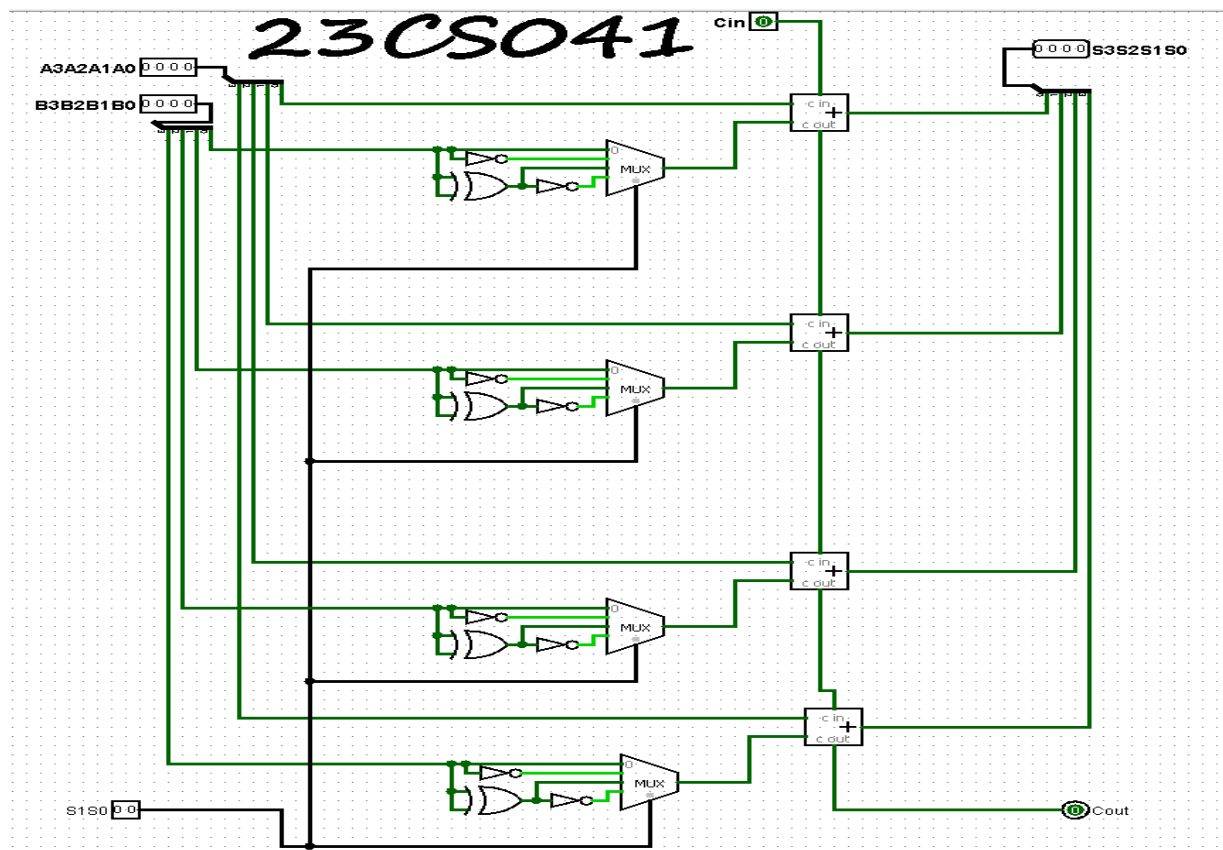

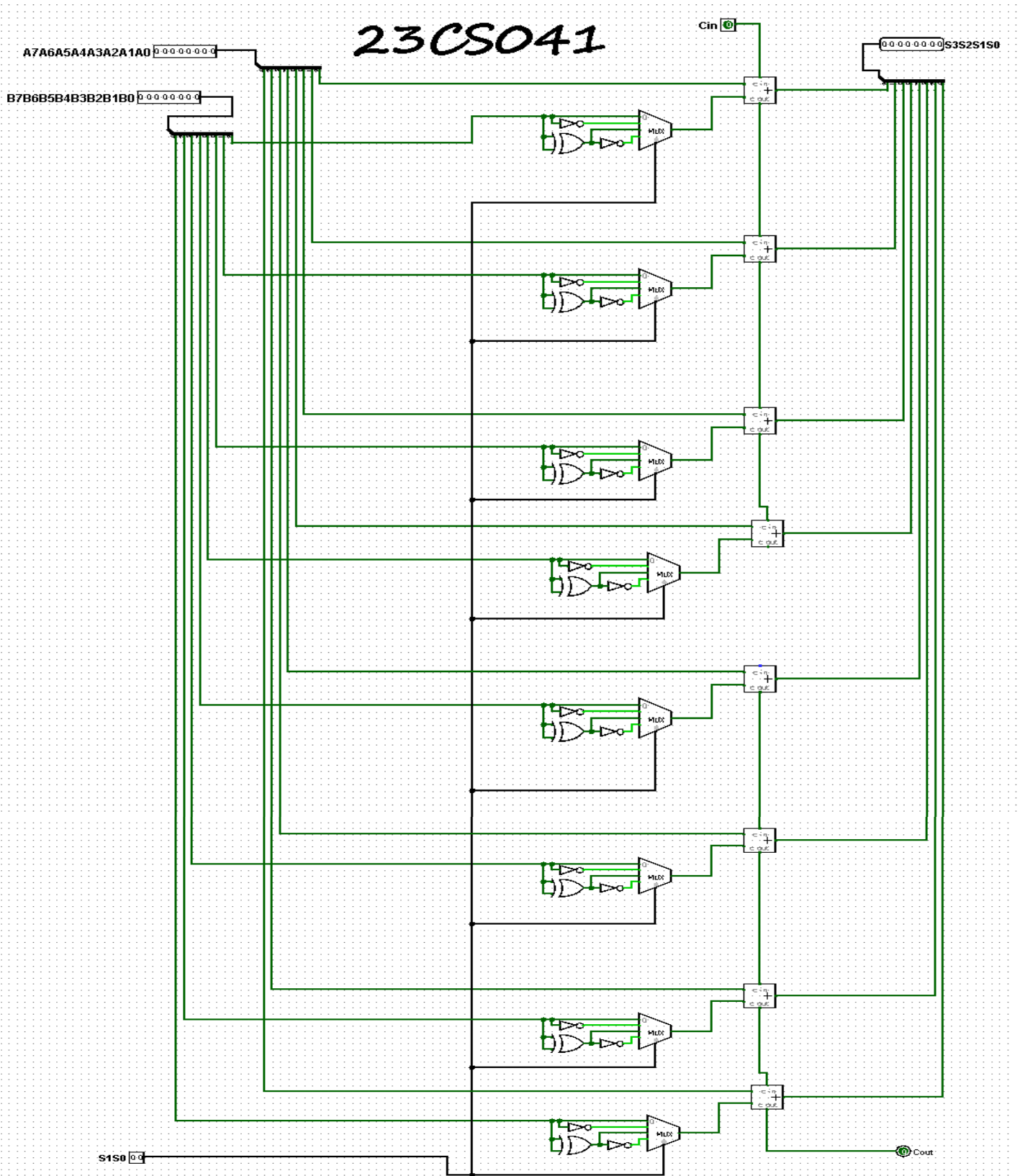
**4) 8-bit arithmetic**


**ii. 1) 1-bit logical**


# 23CS041

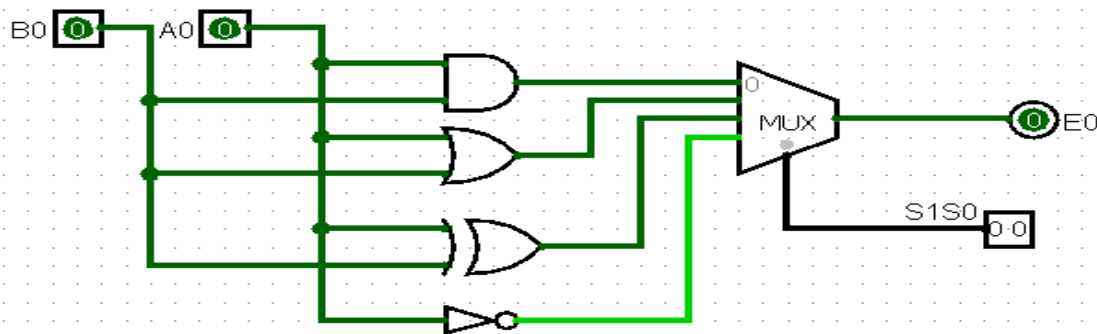**2) 2-bit logical**


# 23CS041

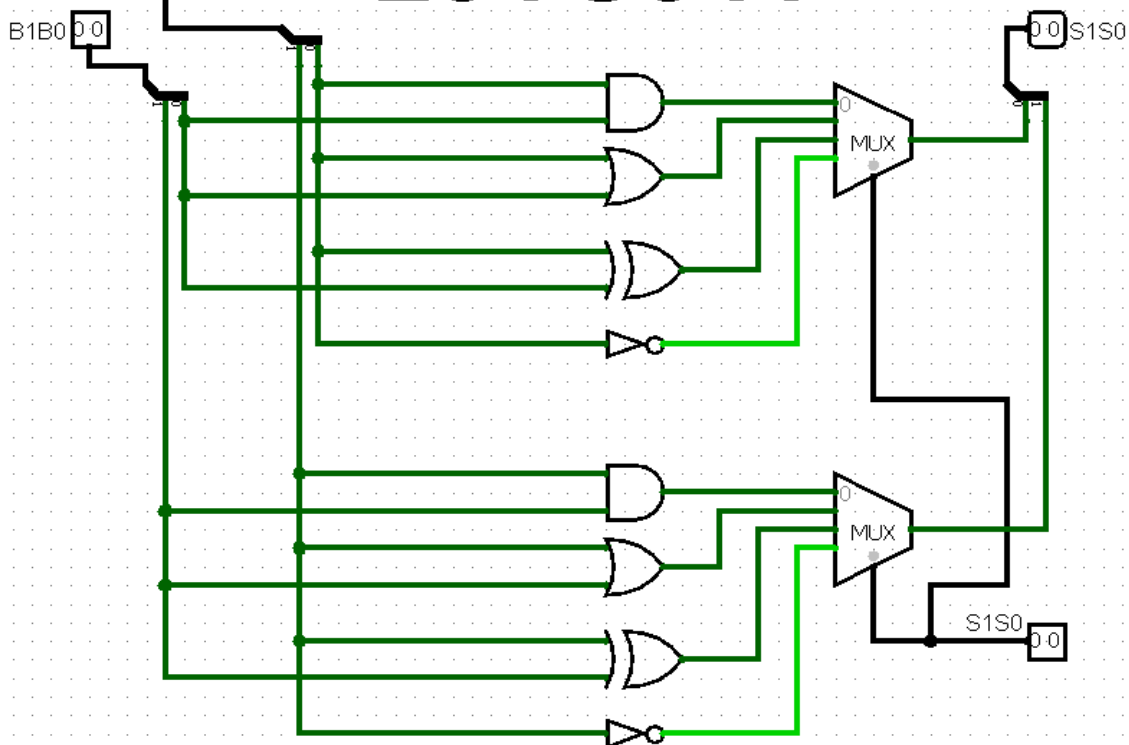


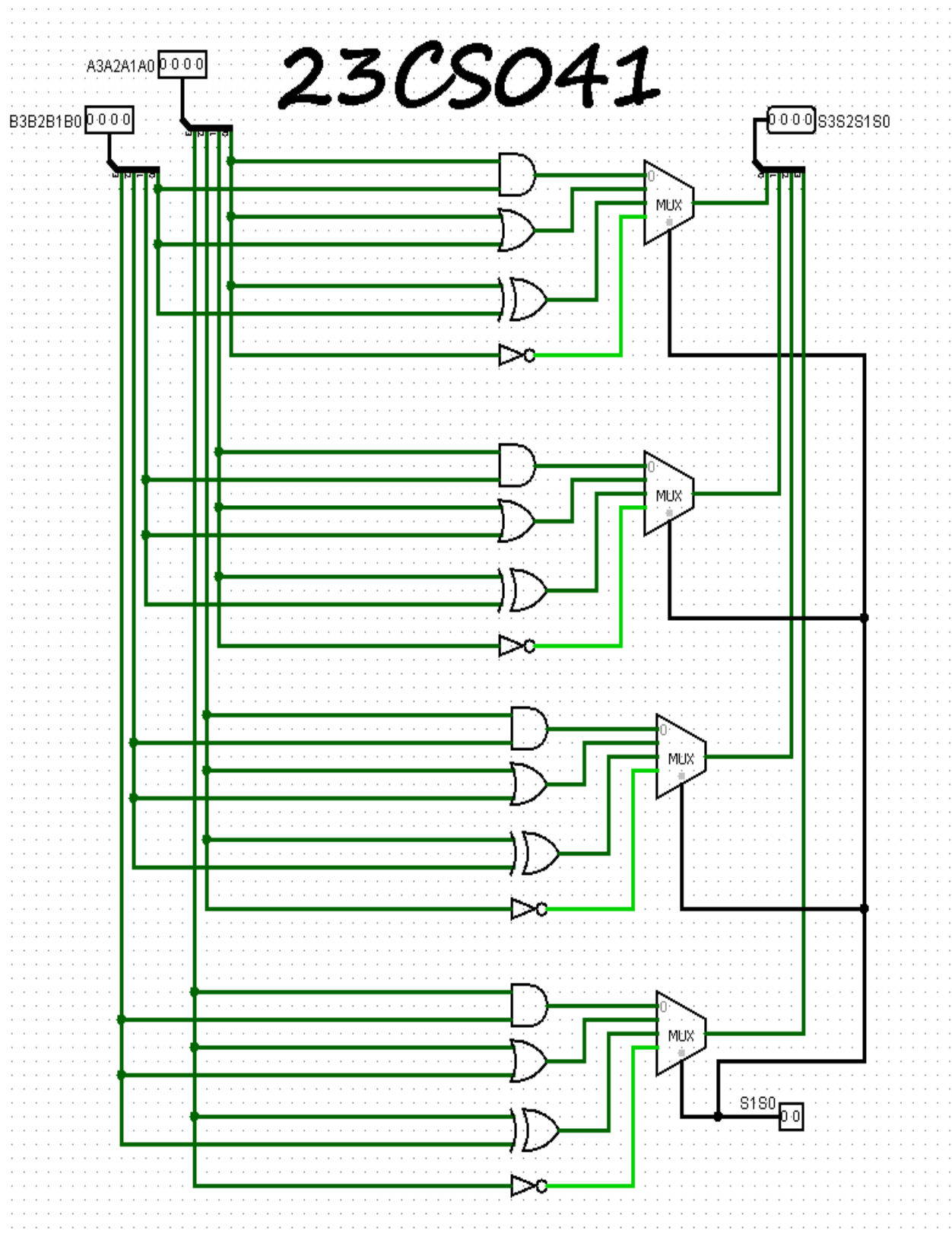**3) 4-bit logical**


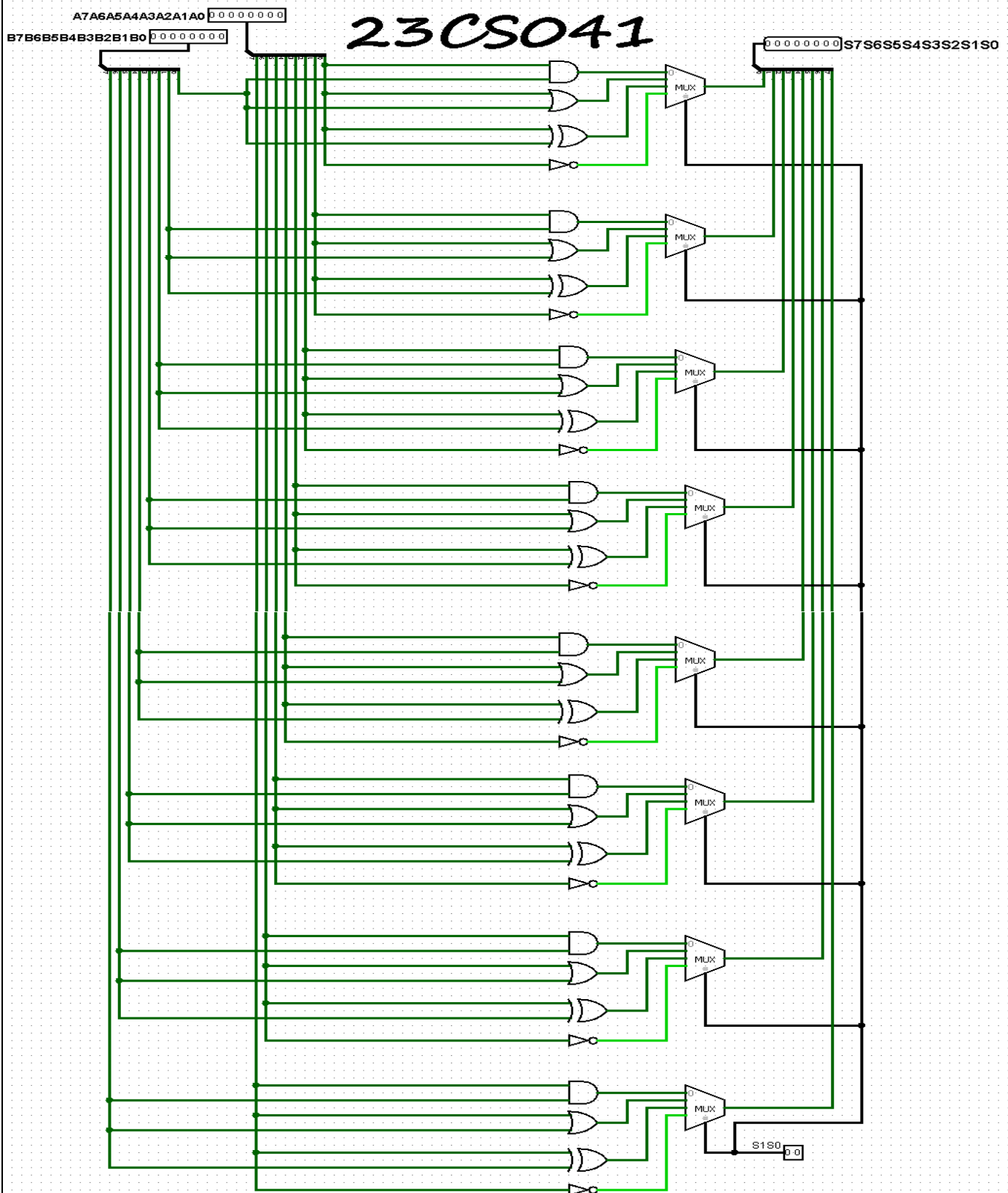
**4) 8-bit logical**


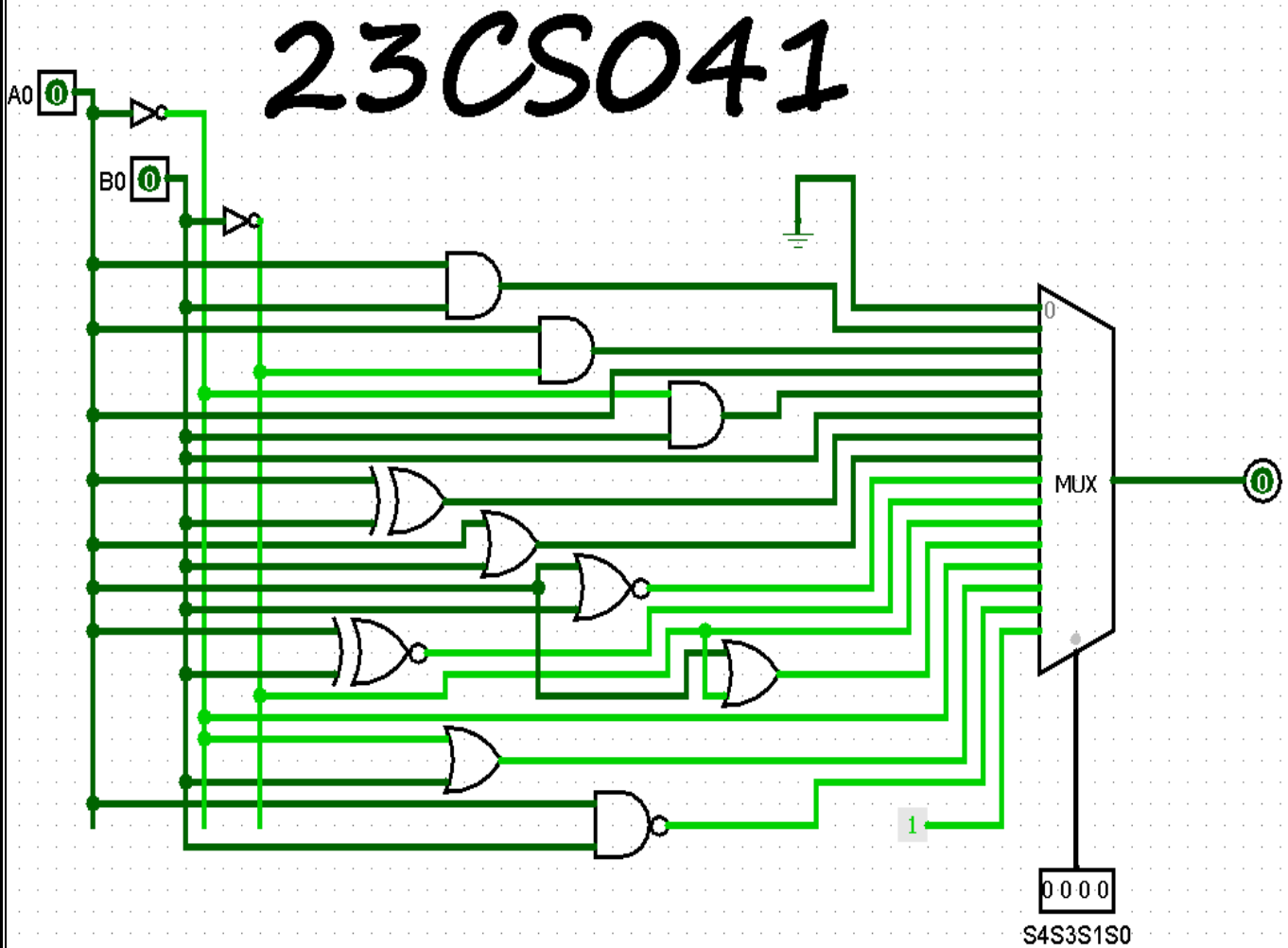
iii. 1) 1-bit logical circuits for sixteen logical functions





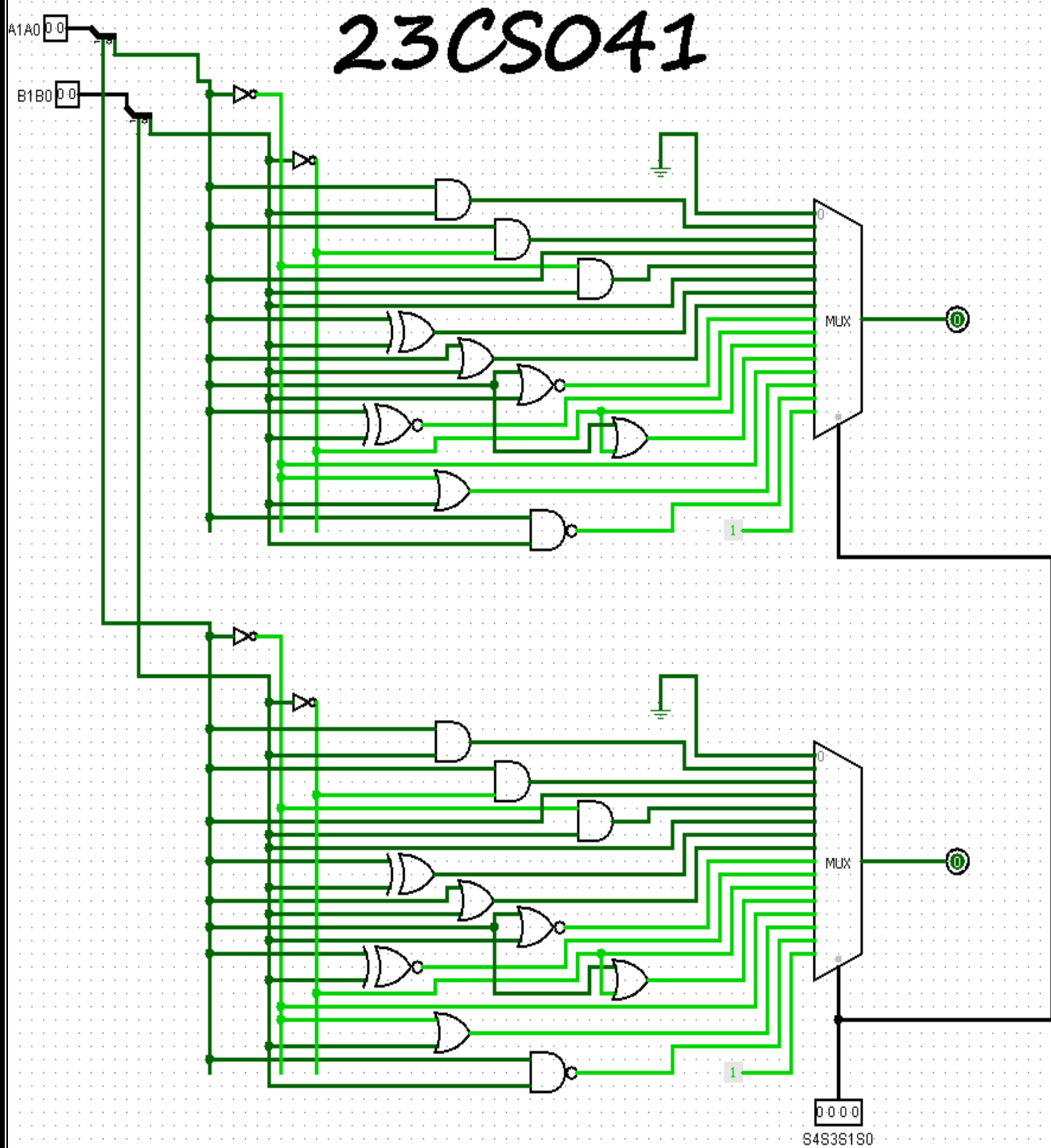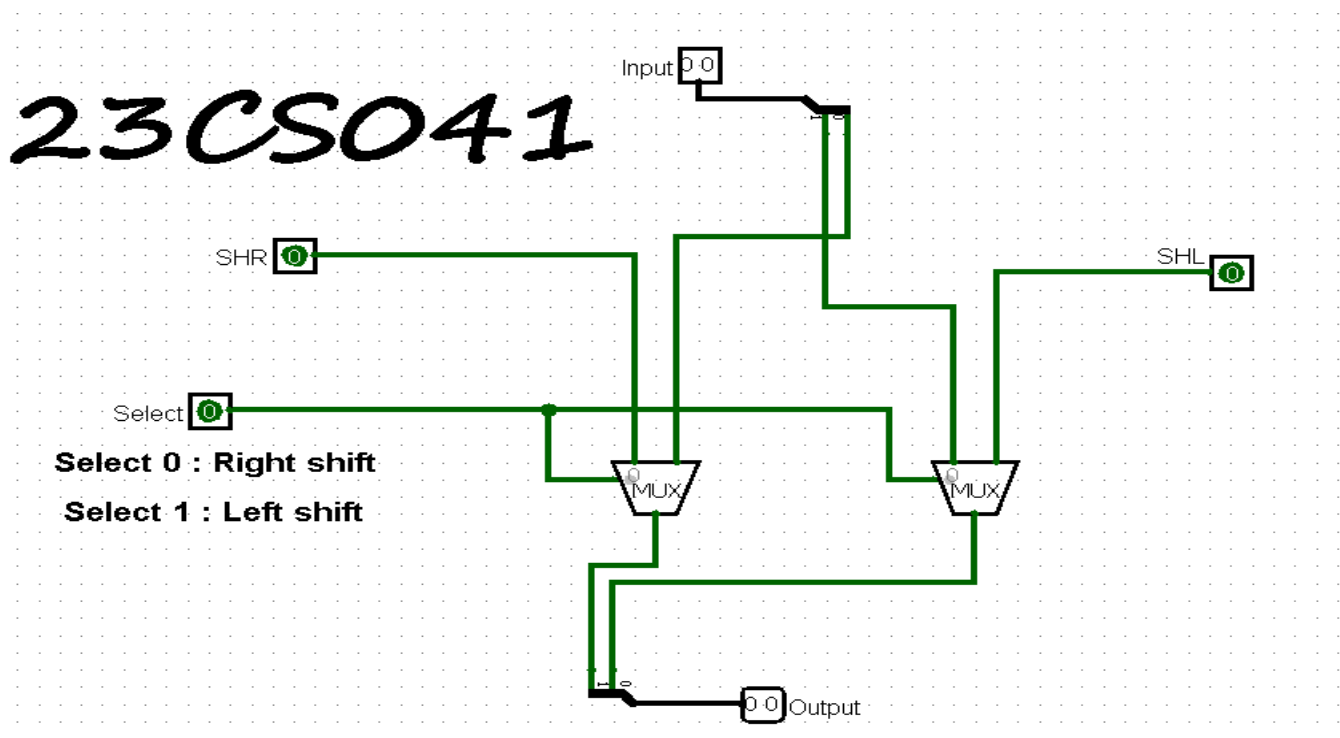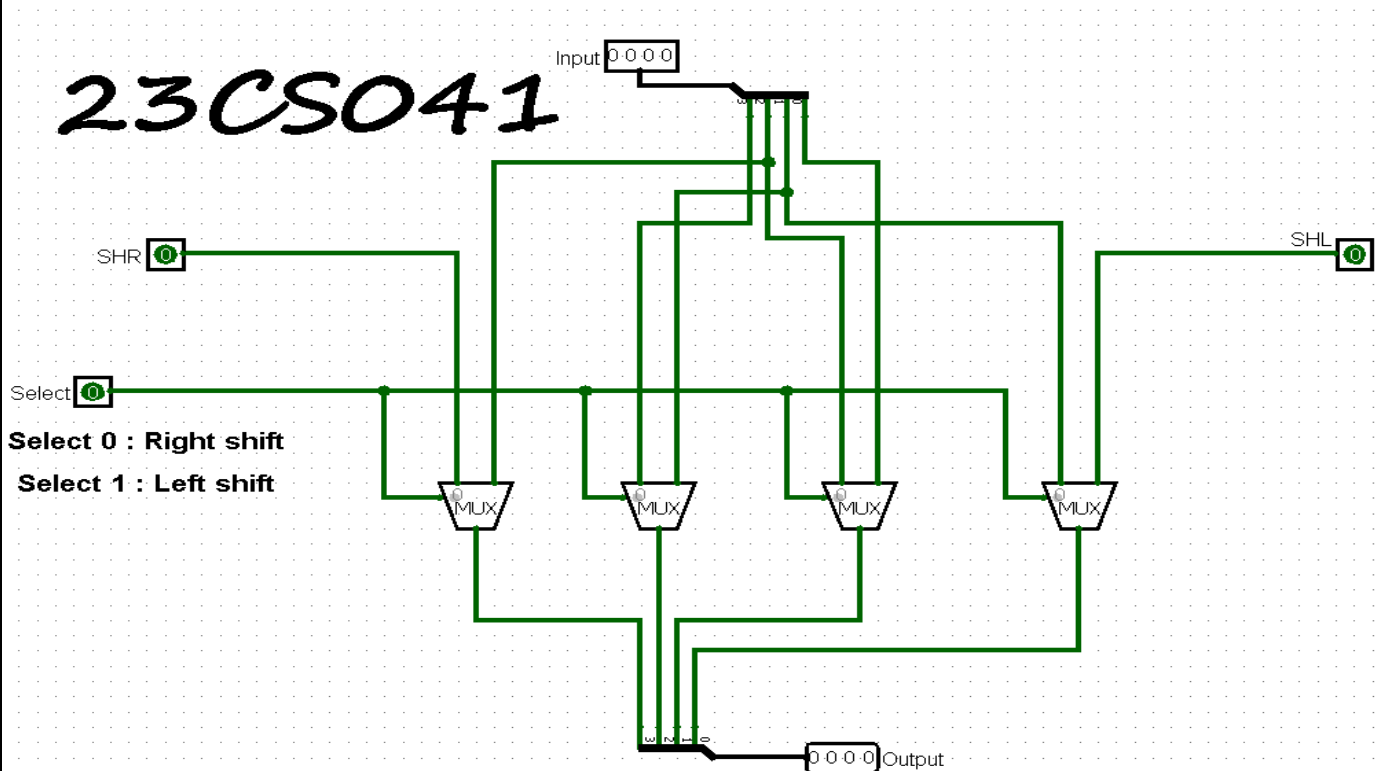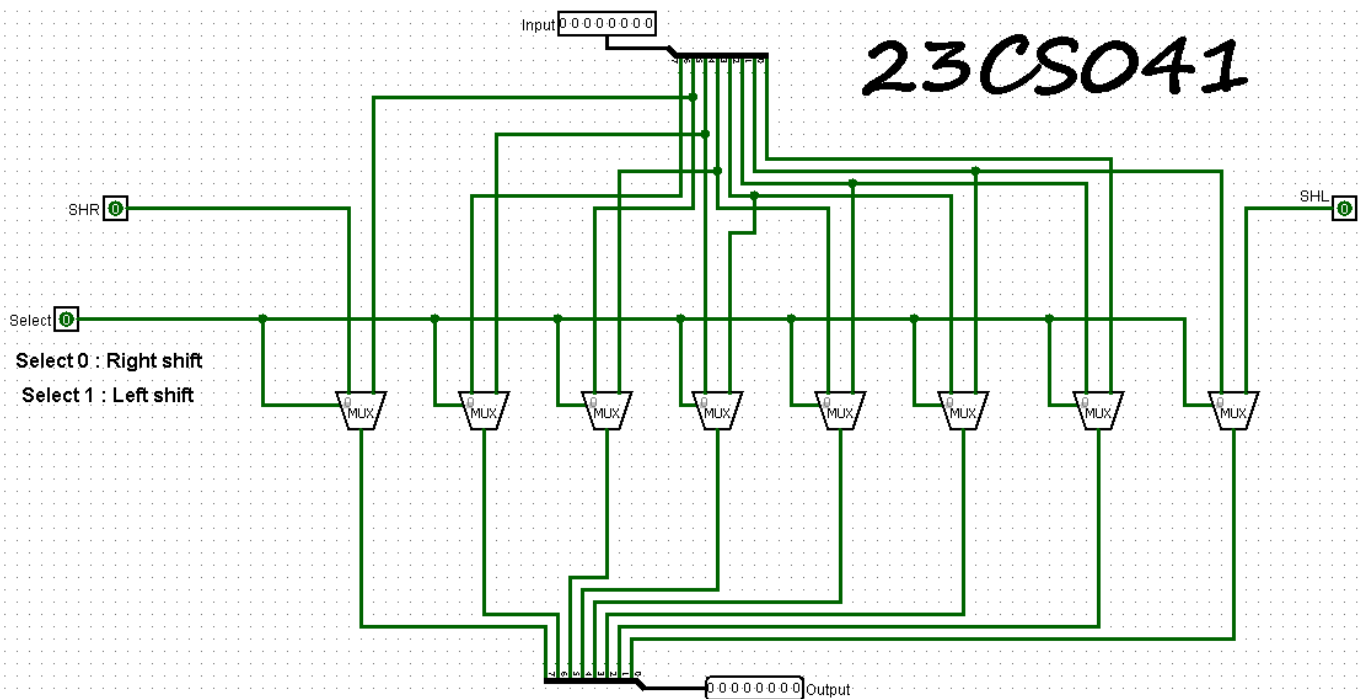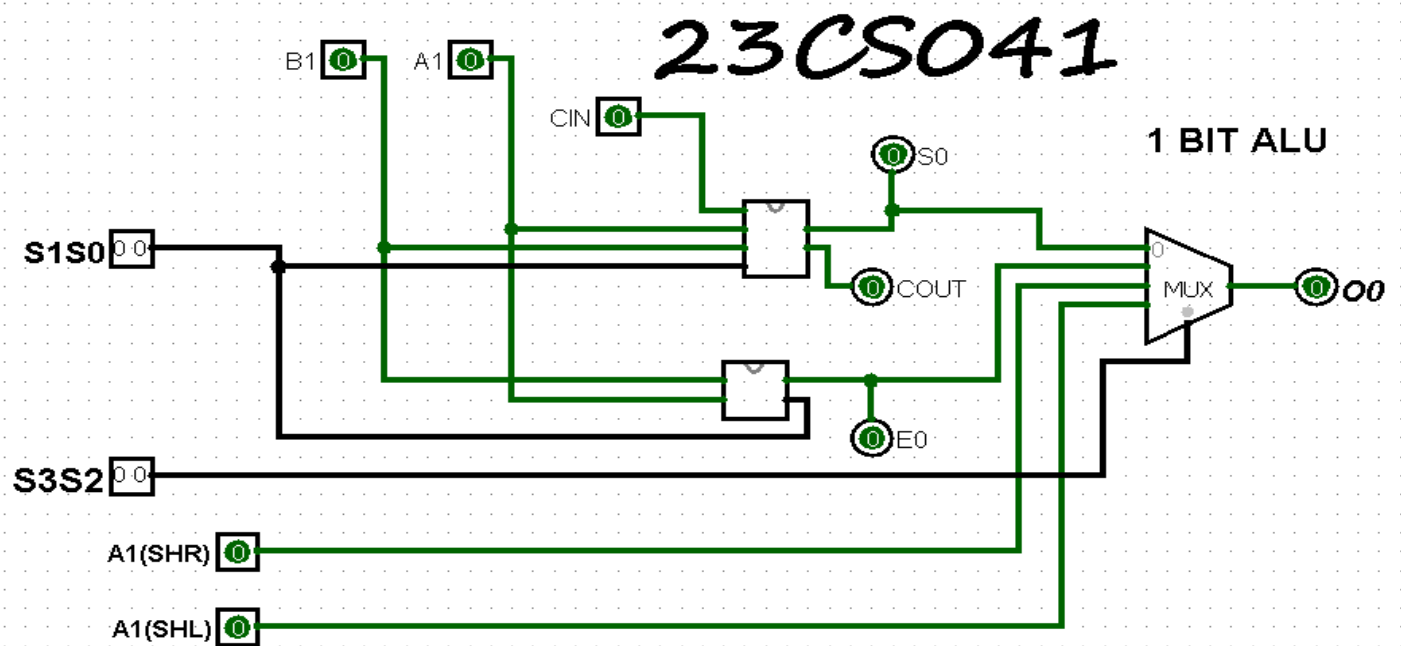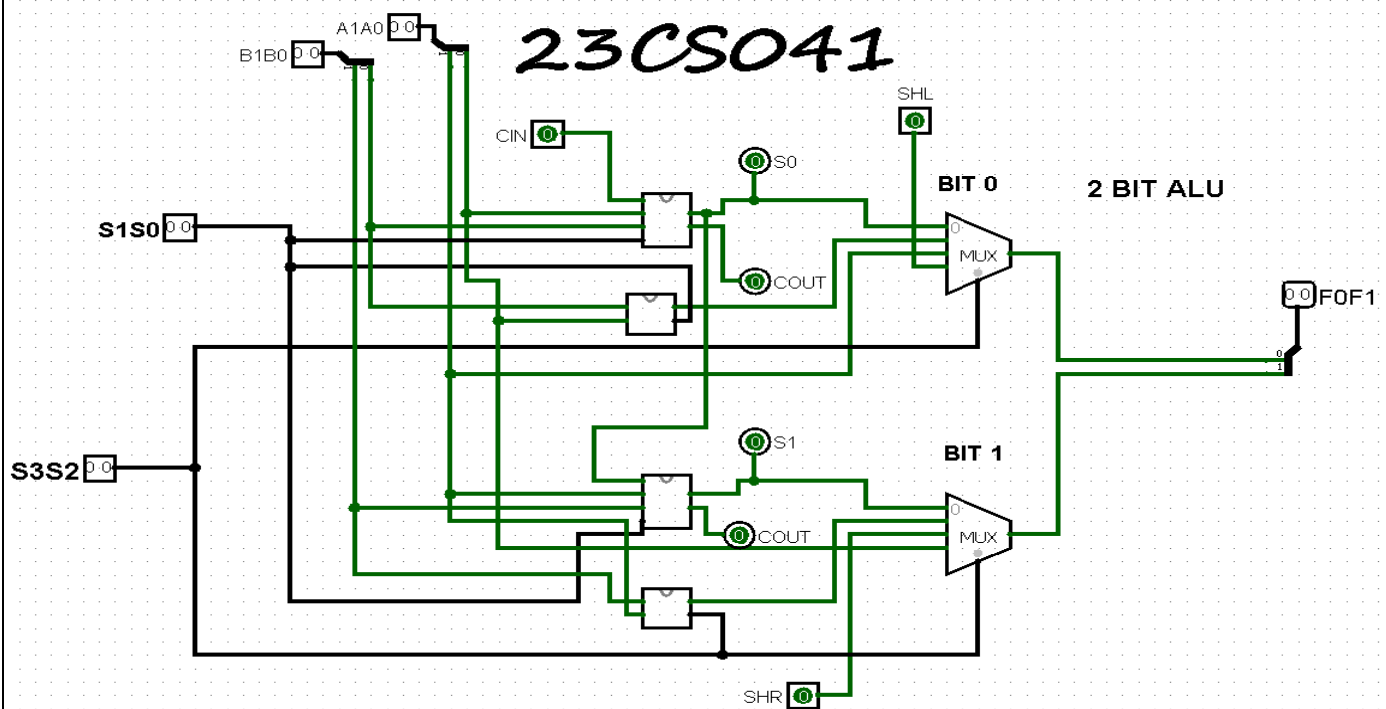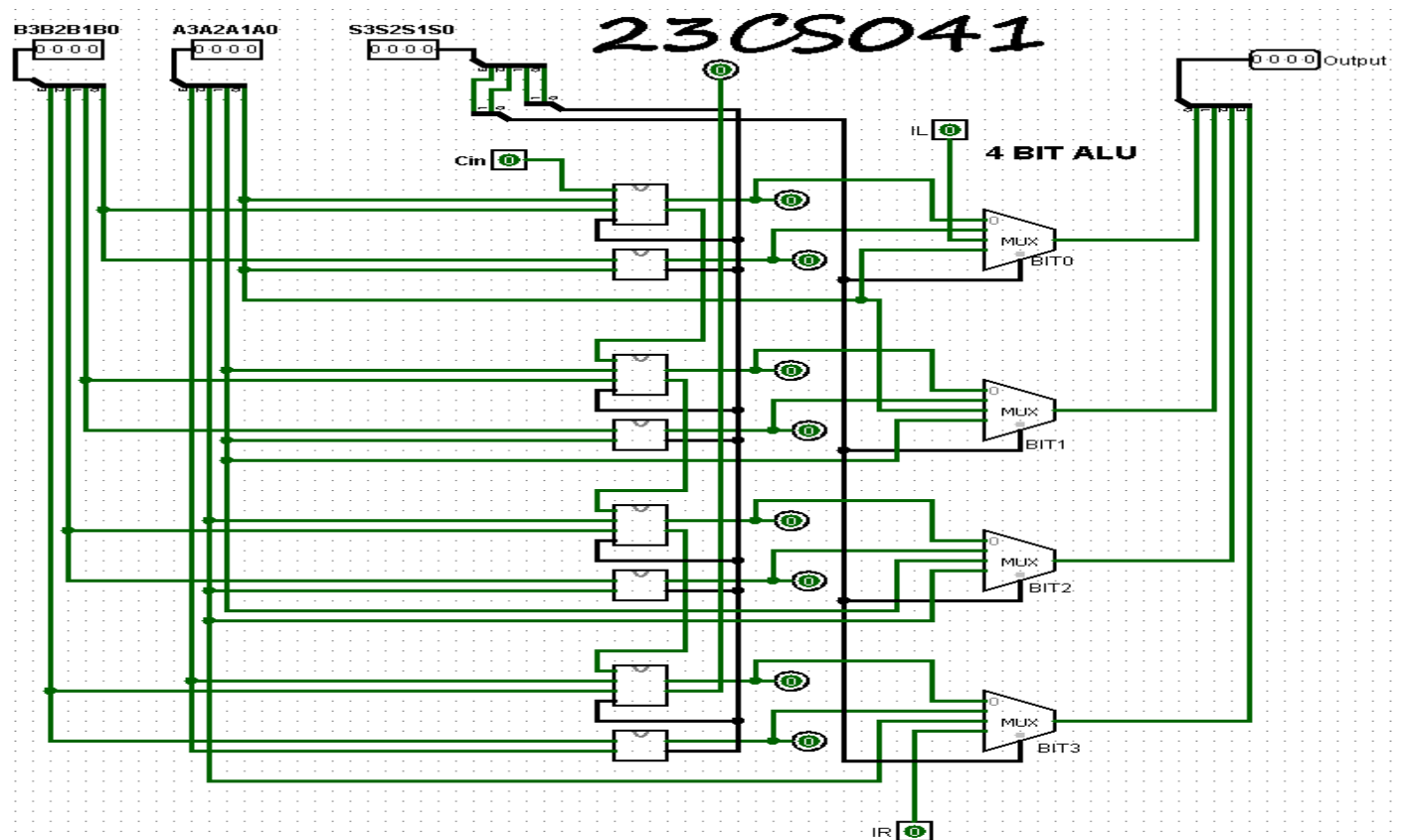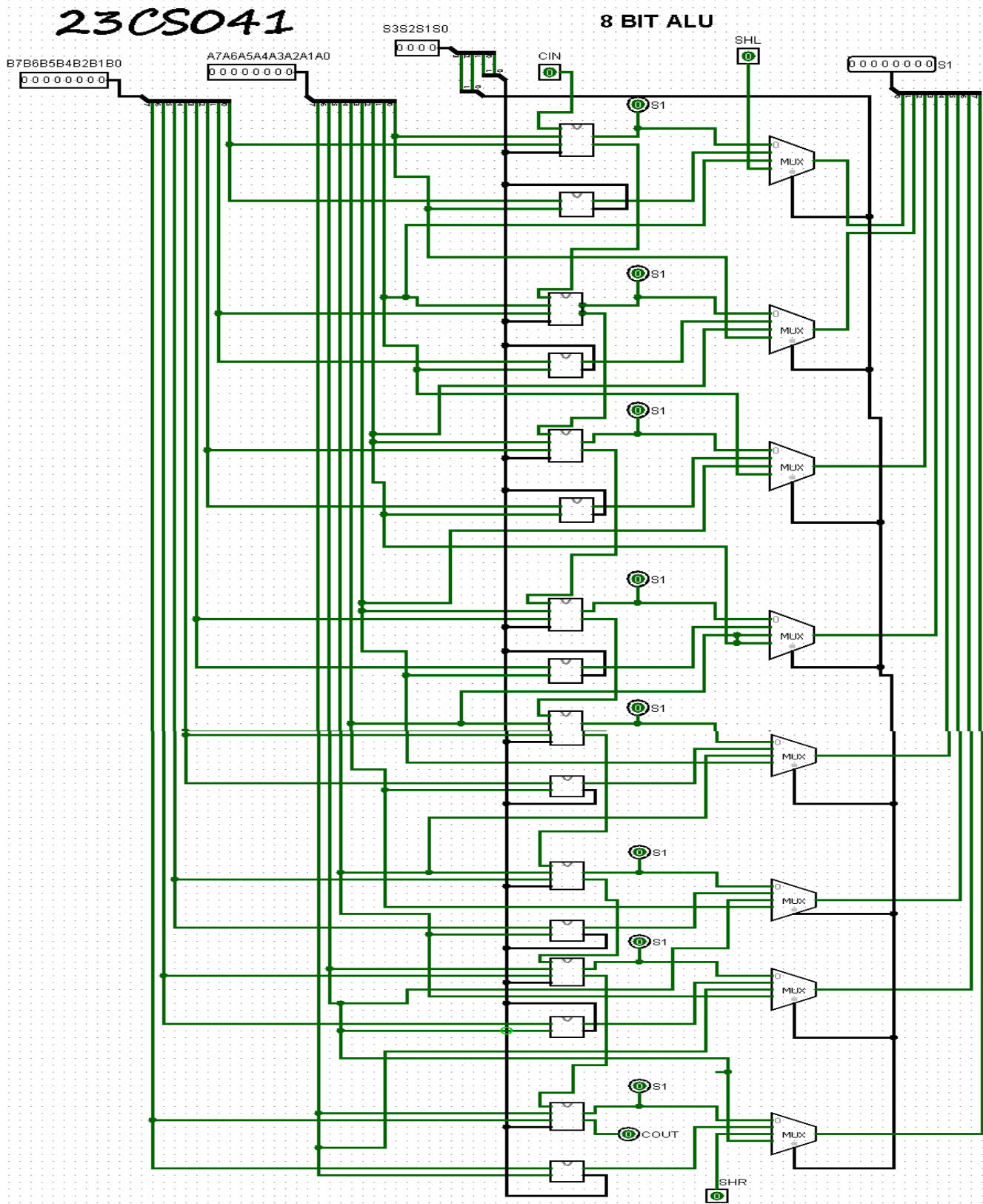
**2) 2-bit logical circuits for sixteen logical functions**

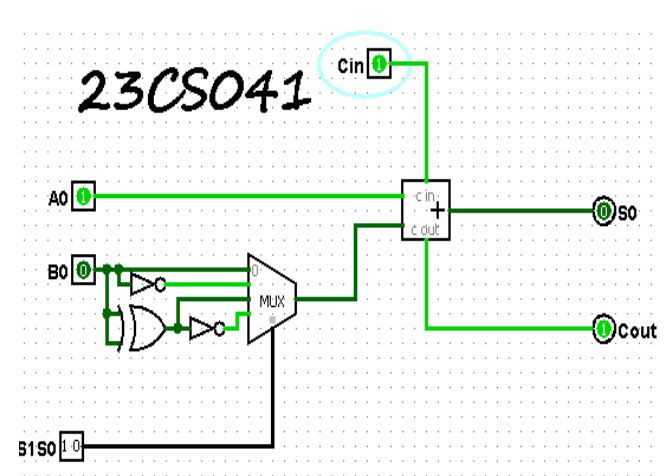
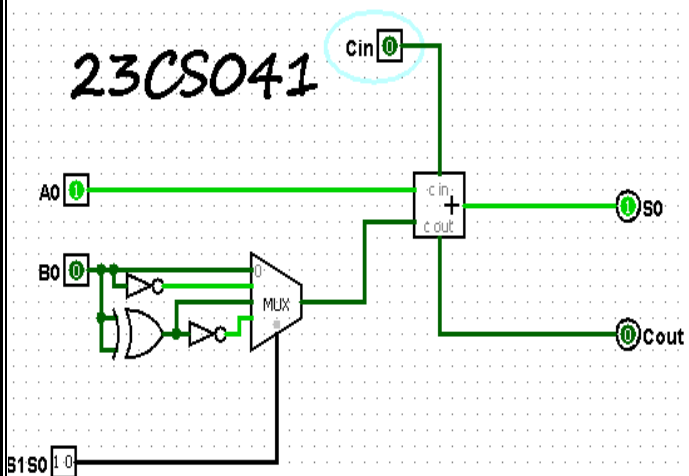
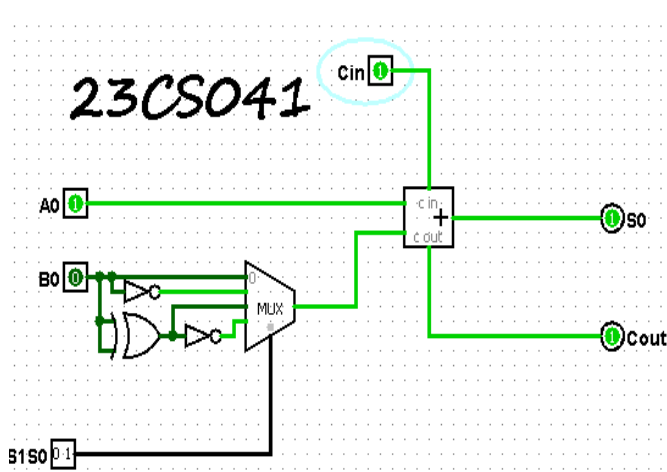
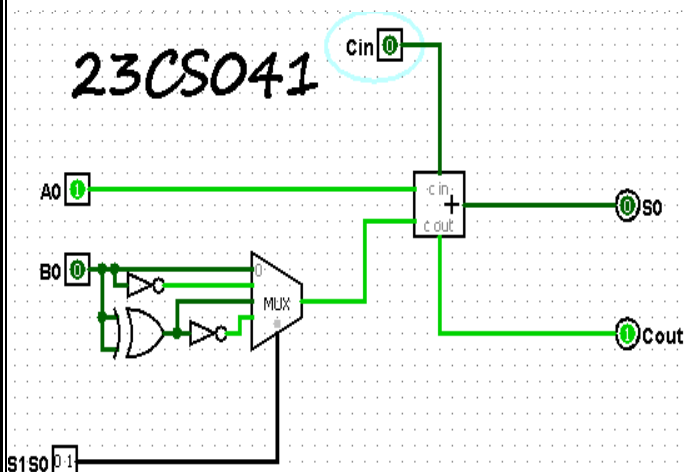
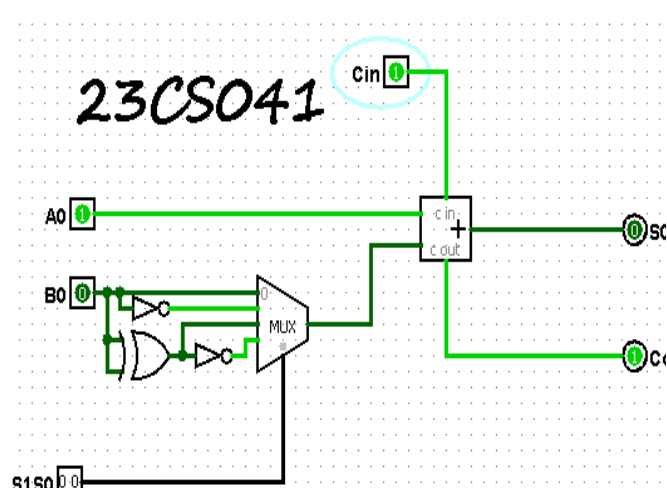
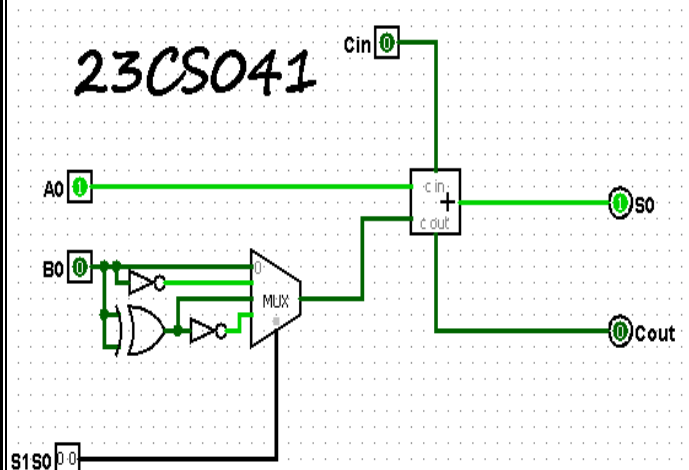



**iv. 1) 2-bit bidirectional shifter****2) 4-bit bidirectional shifter**

**3) 8-bit bidirectional shifter****v. 1) 1-bit ALU**


**2) 2-bit ALU****3) 4-bit ALU**


**4) 8-bit ALU**

**OUTPUTS:****i. 1) 1 bit arithmetic**






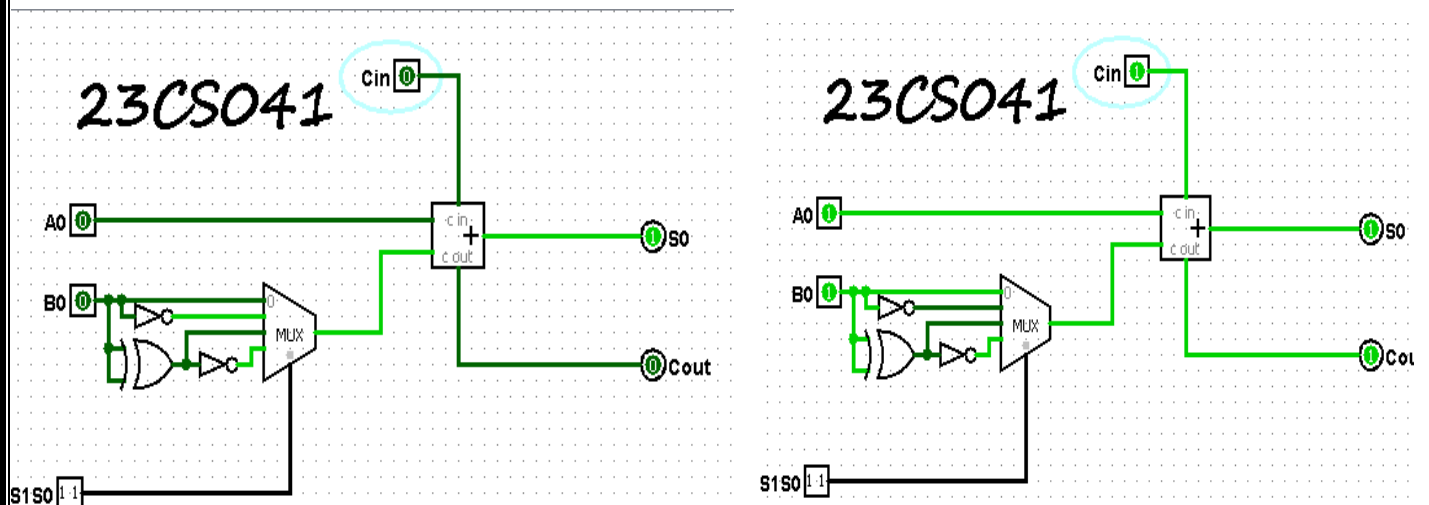


## 2) 4 bit arithmetic

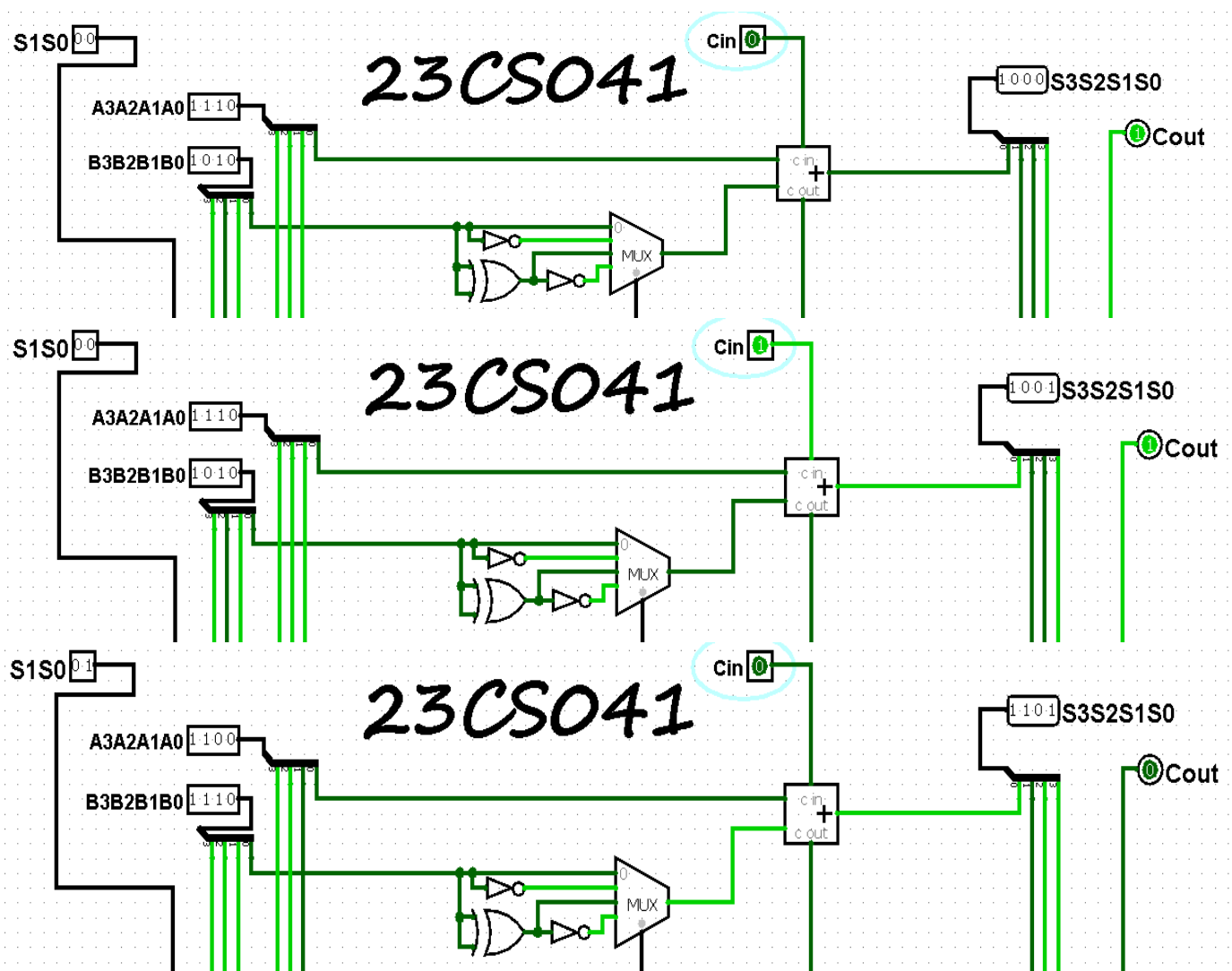


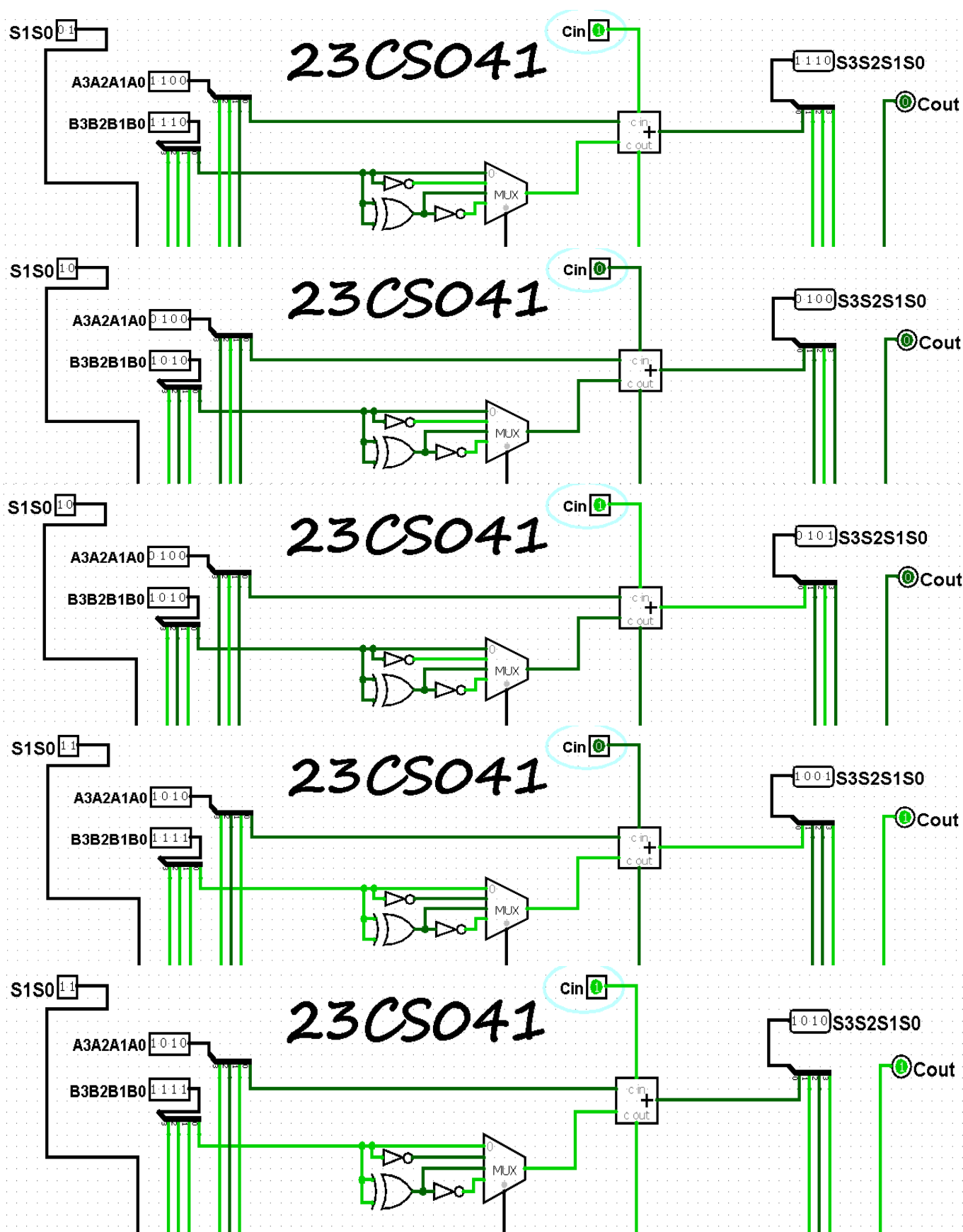


ii. 1) 2 bit logical

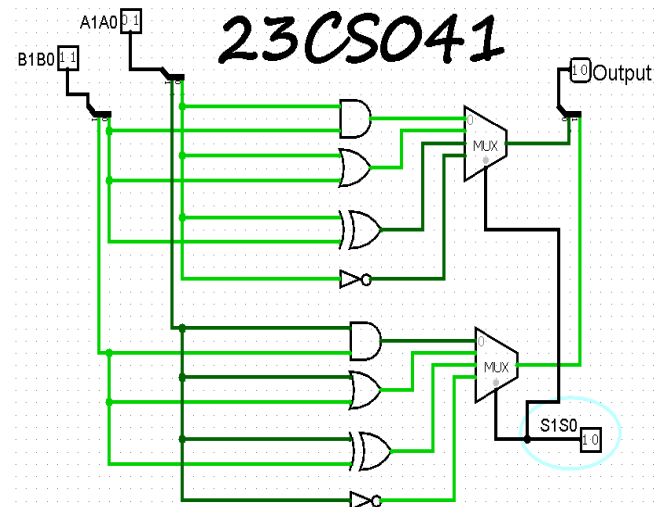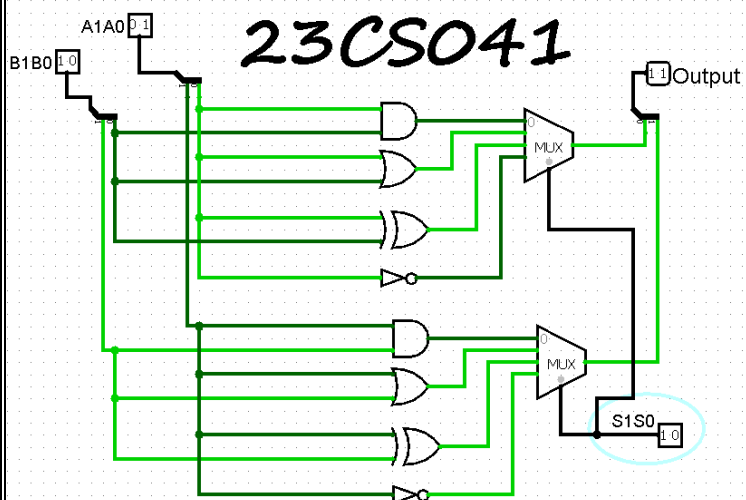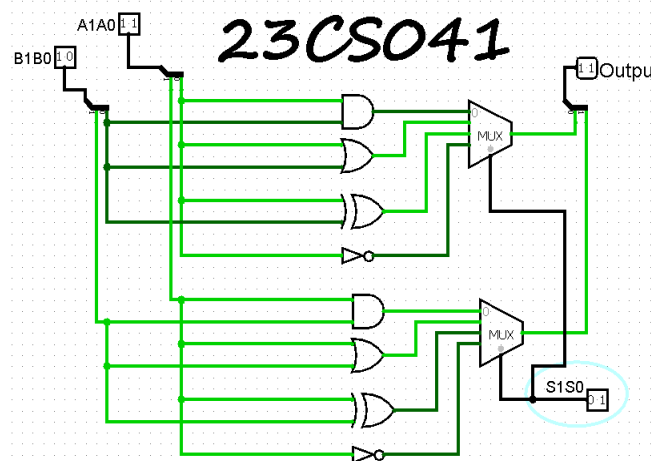
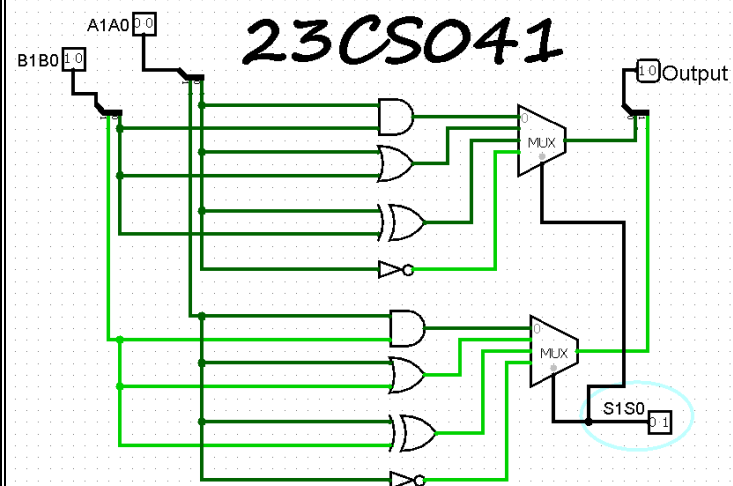
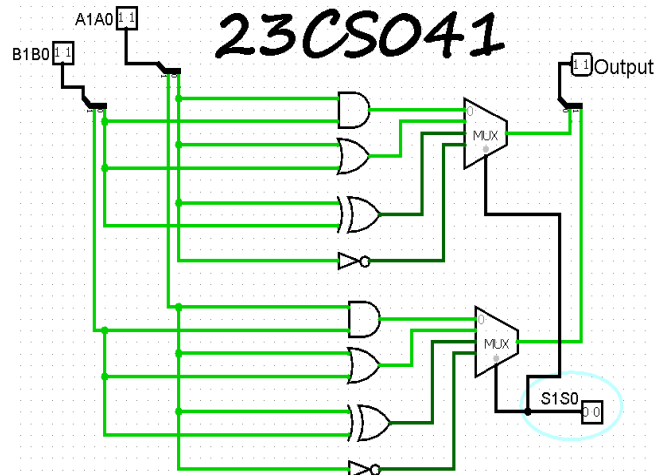
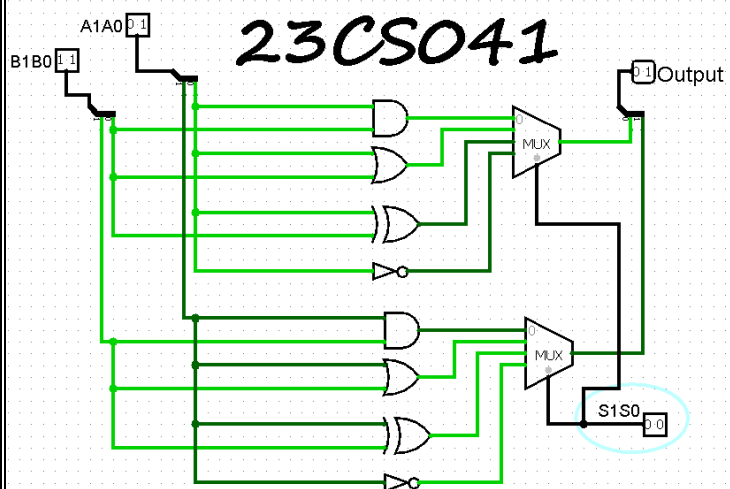




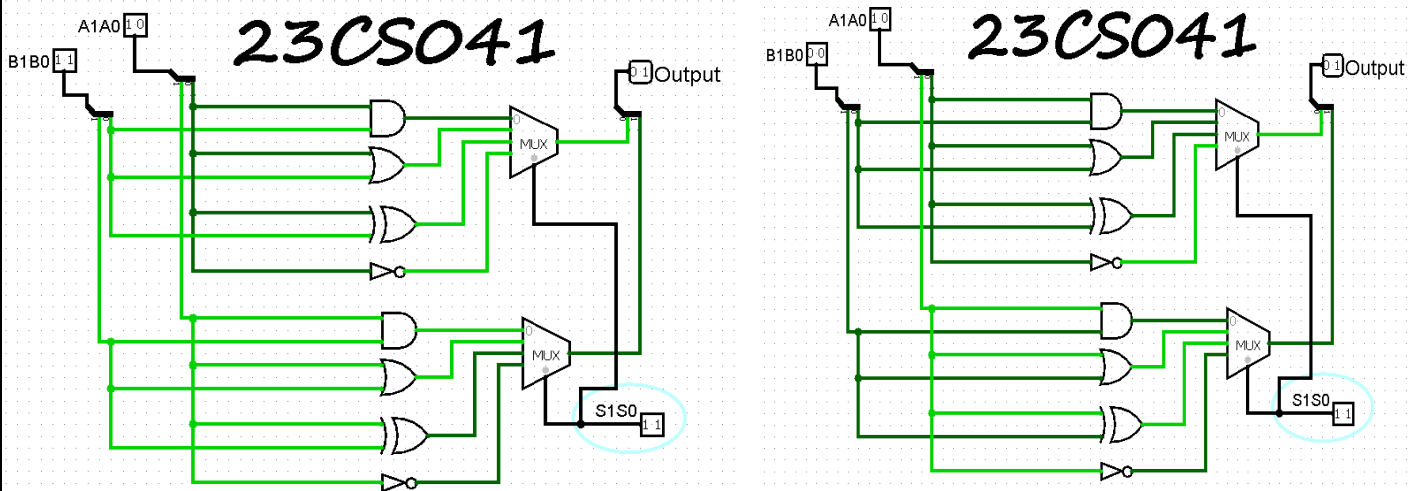







## 2) 8 bit logical





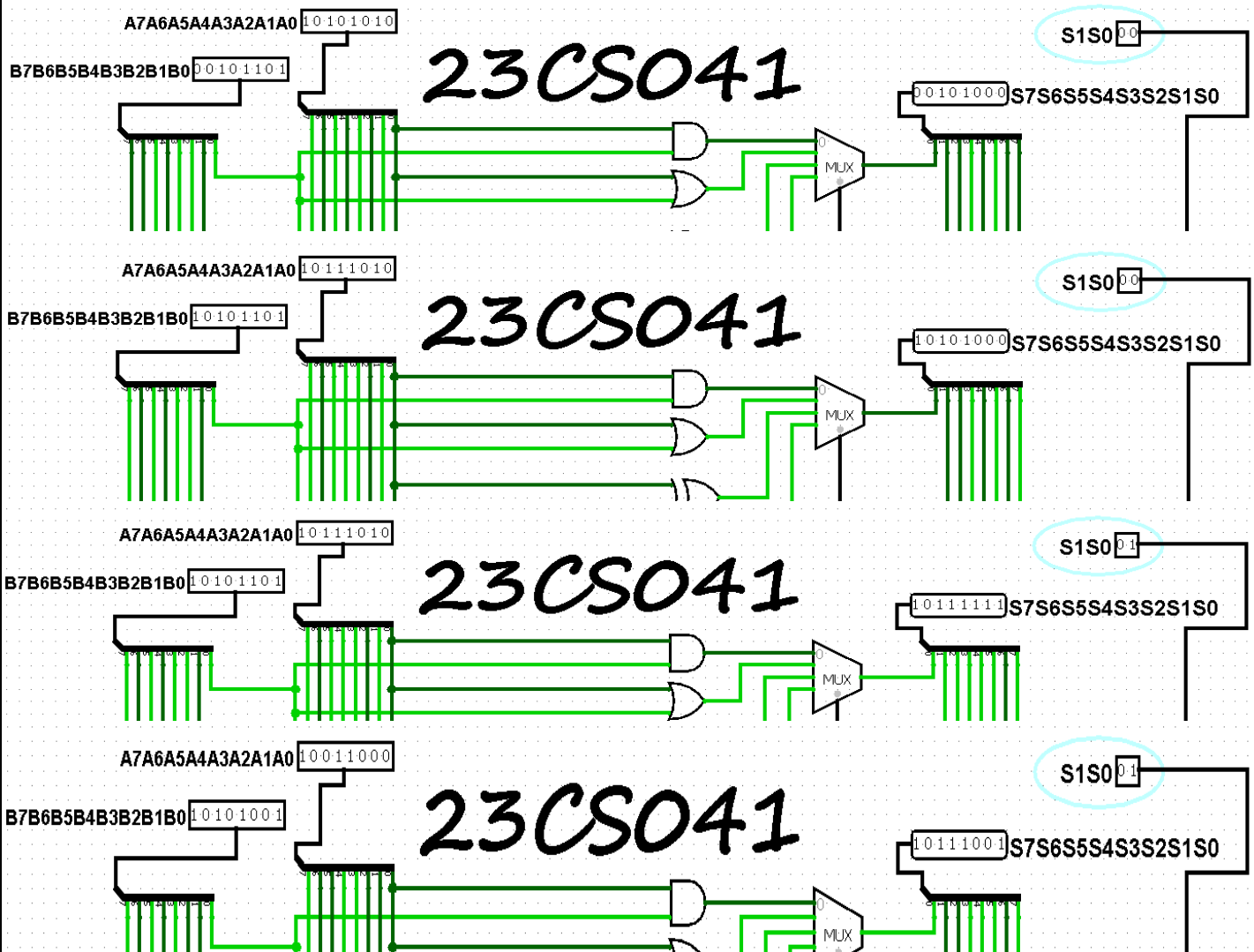



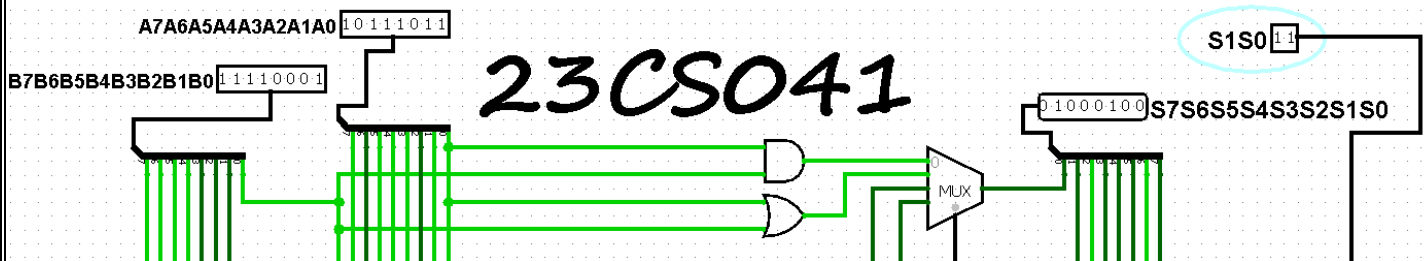
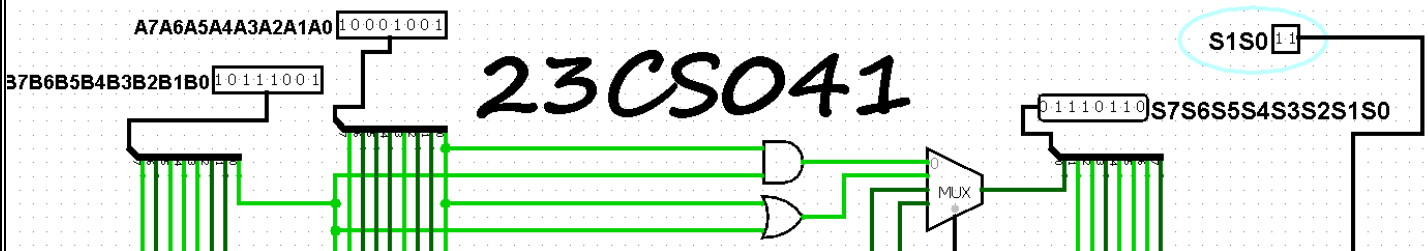
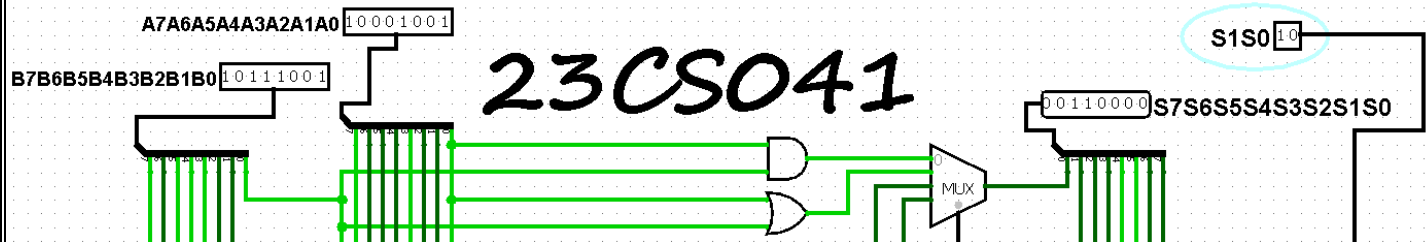
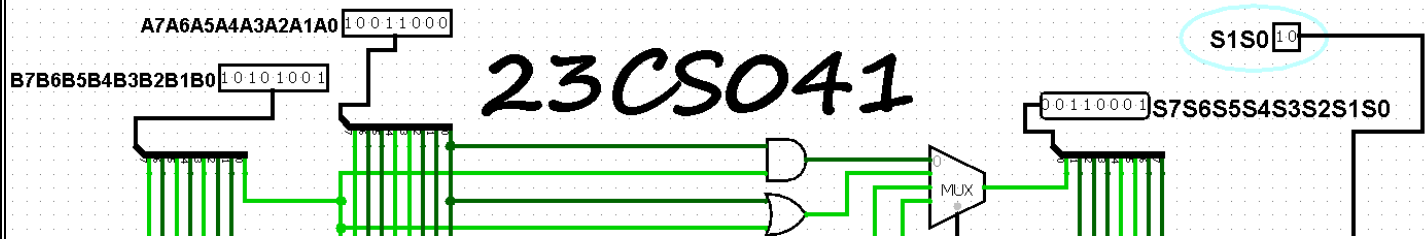








iii. 1) 1-bit 16 logical functions


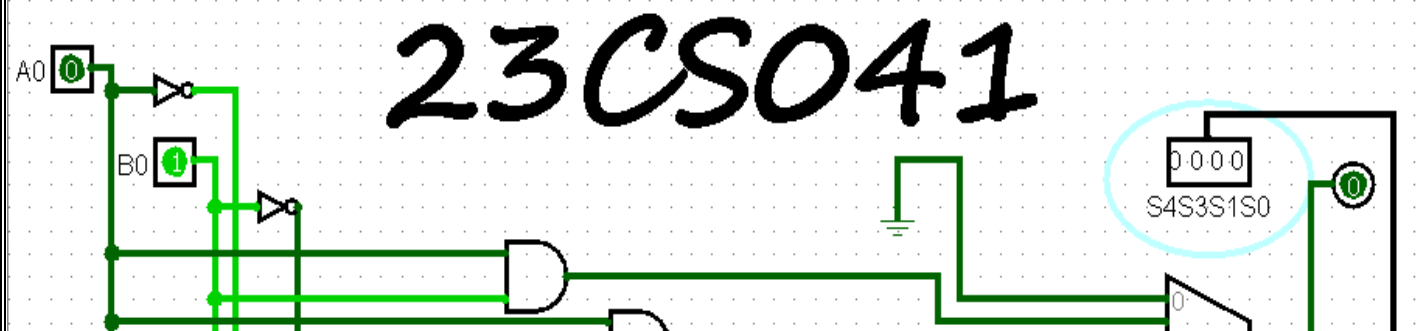


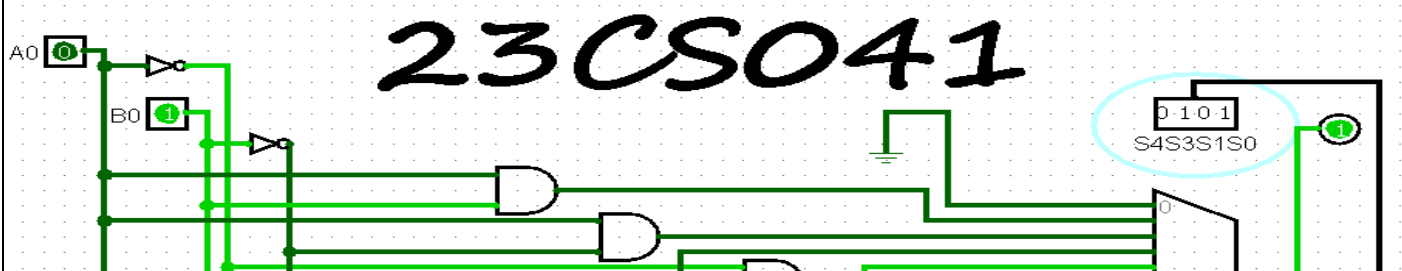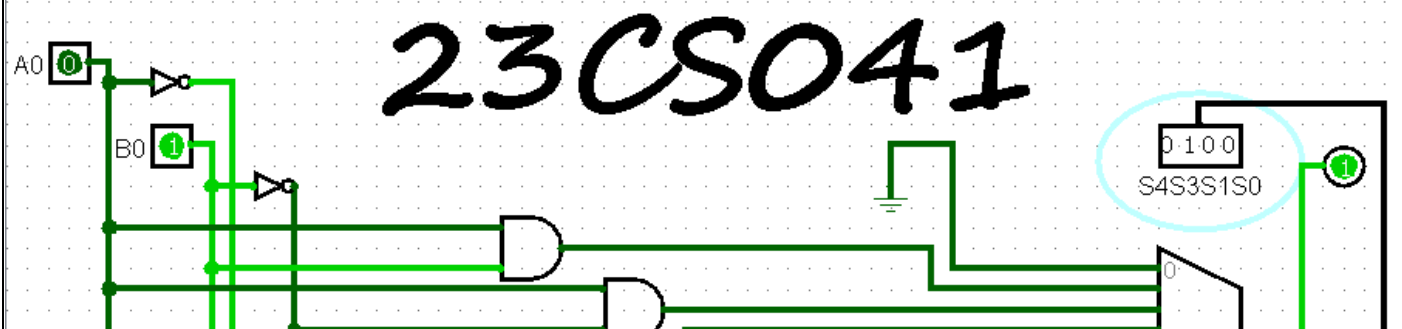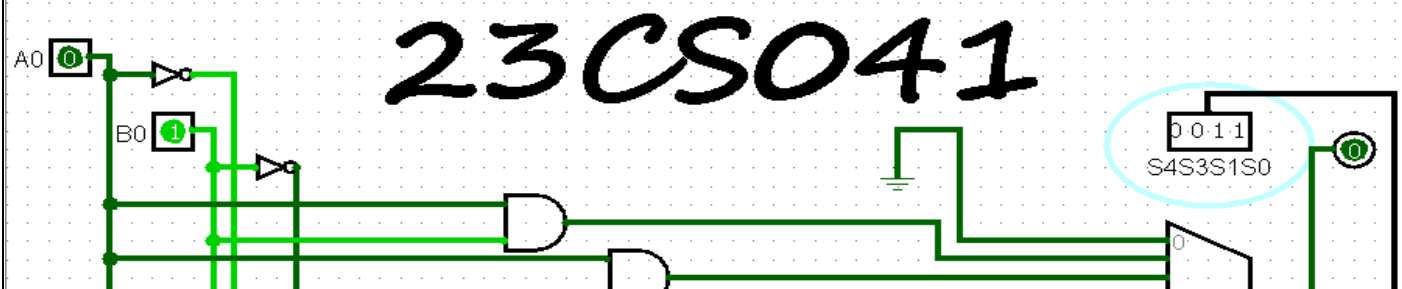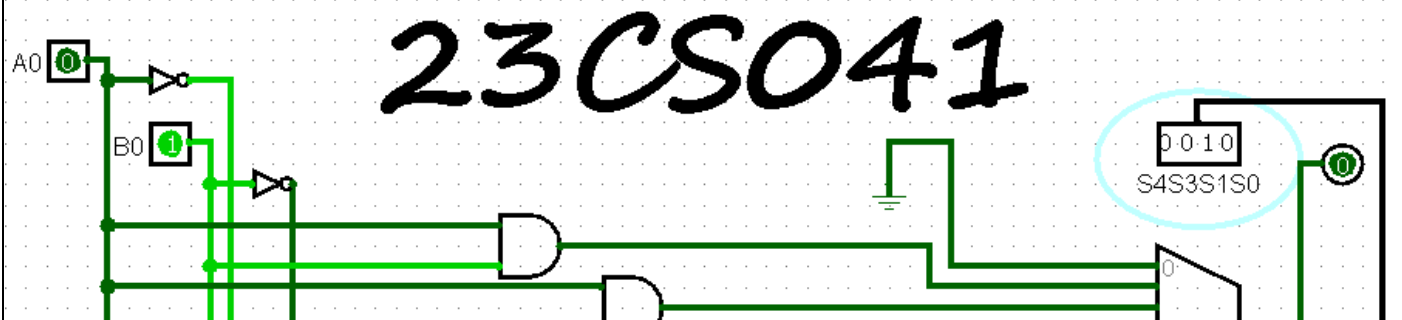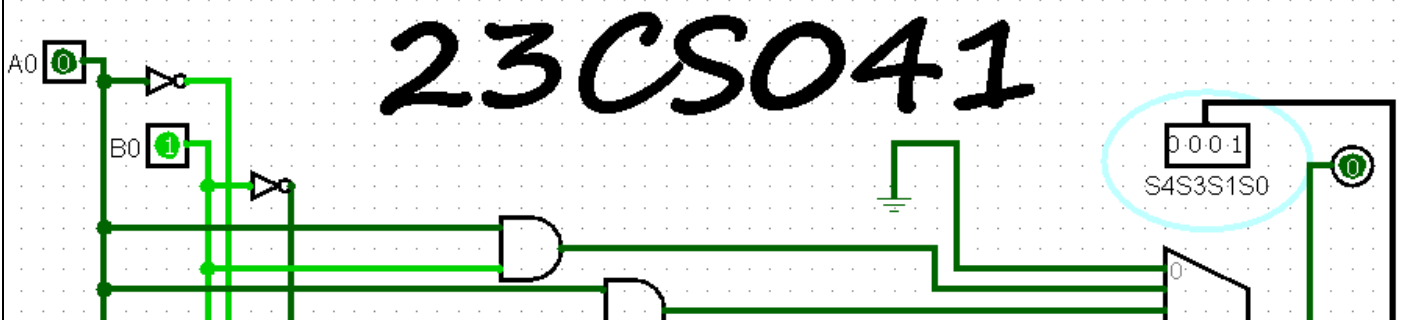

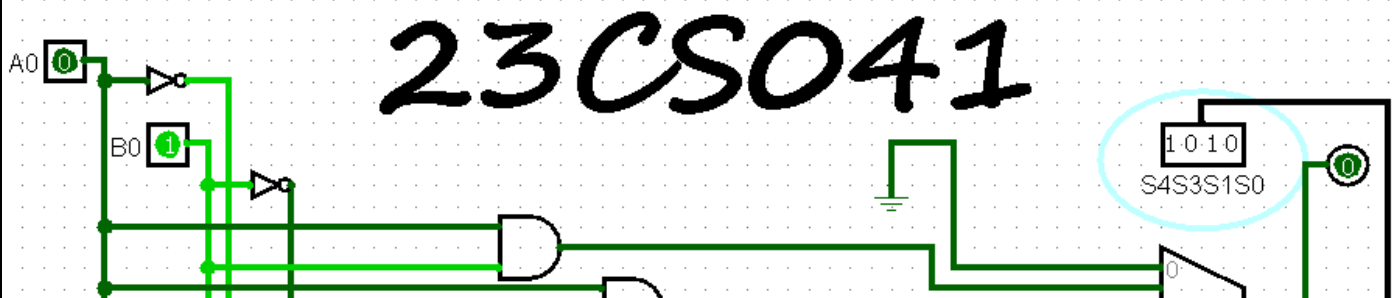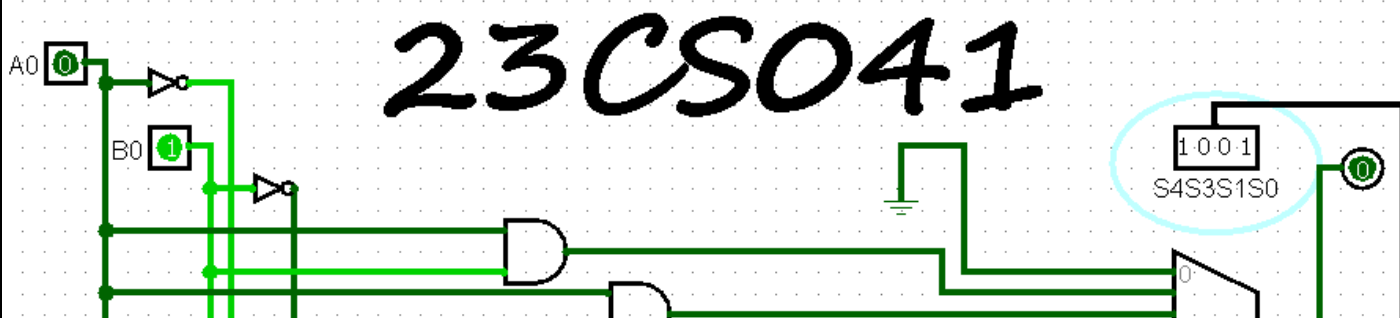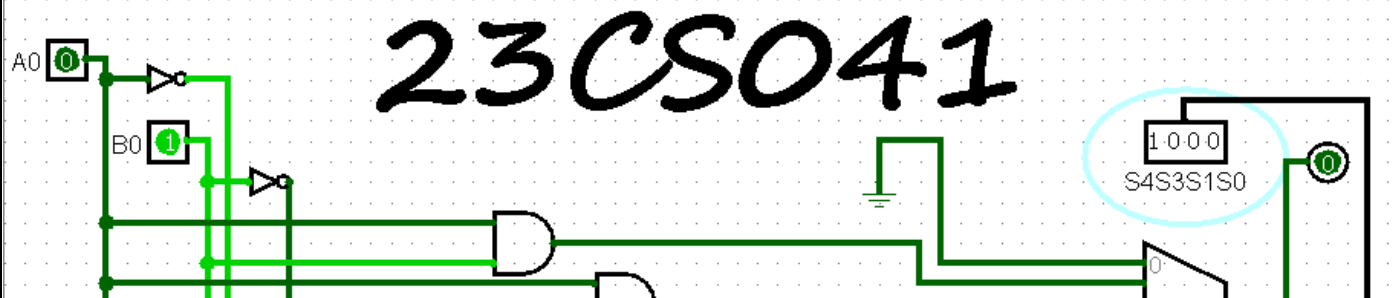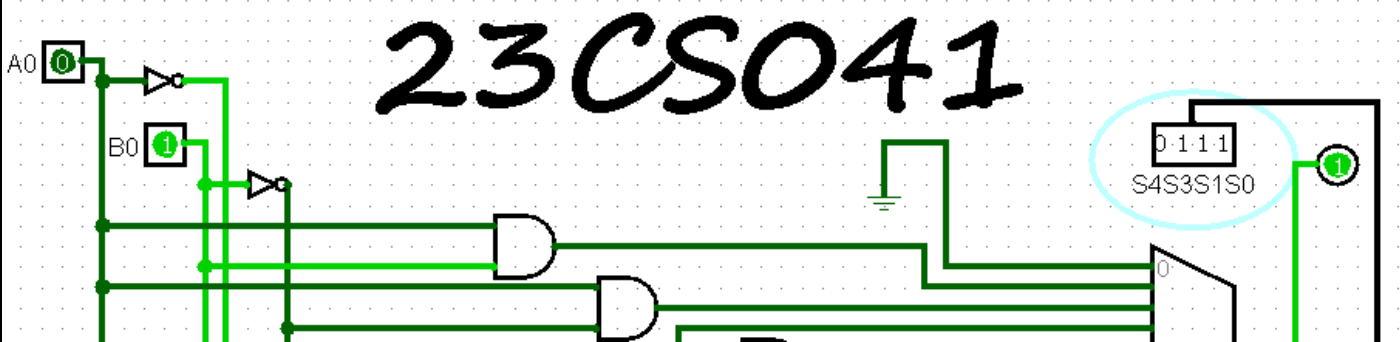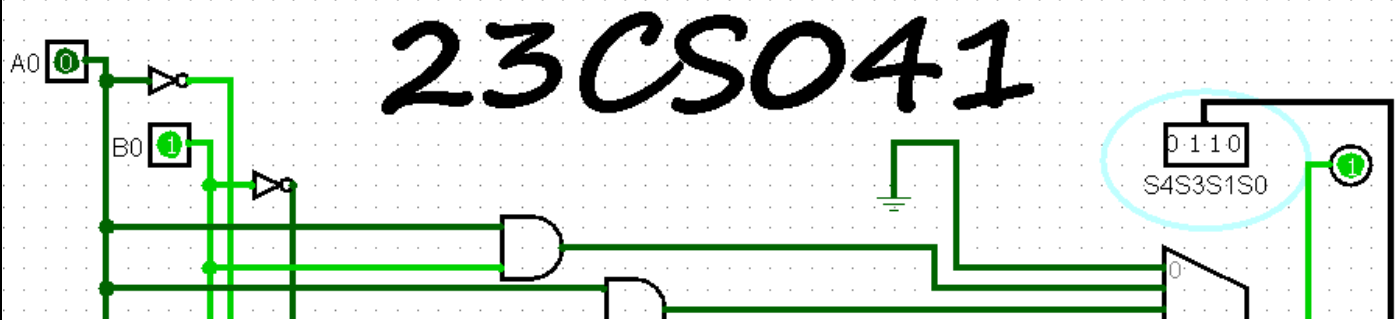


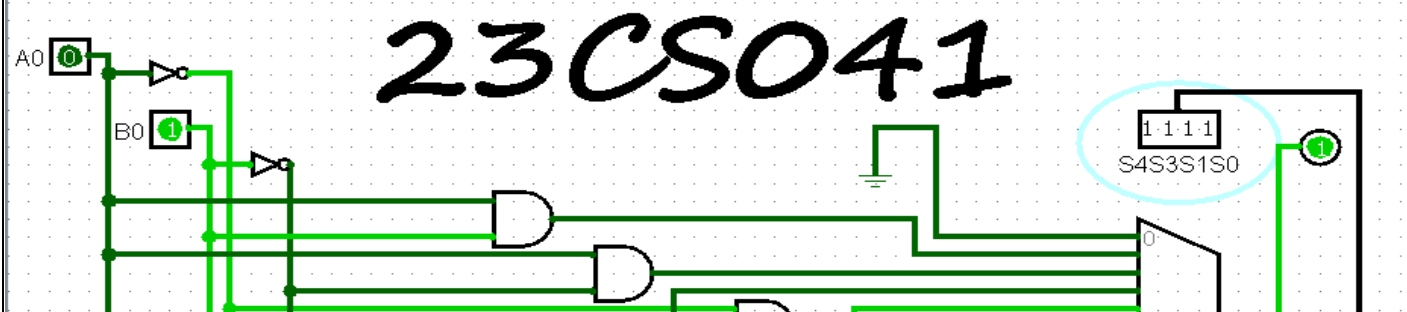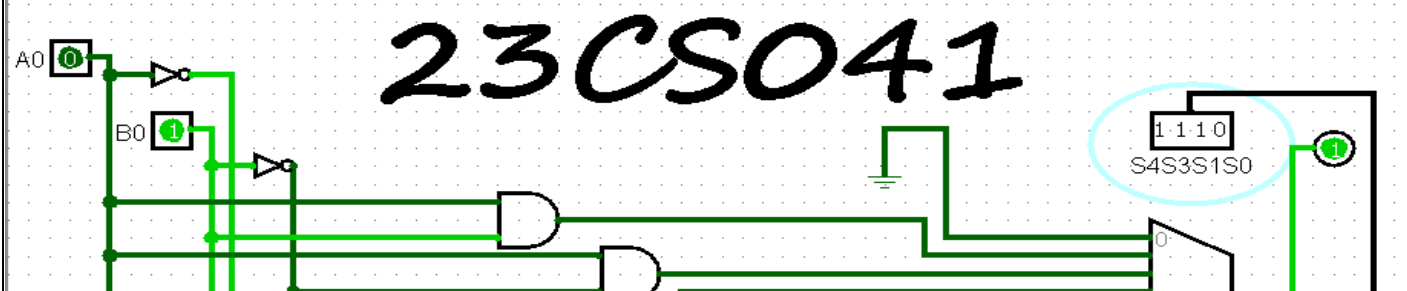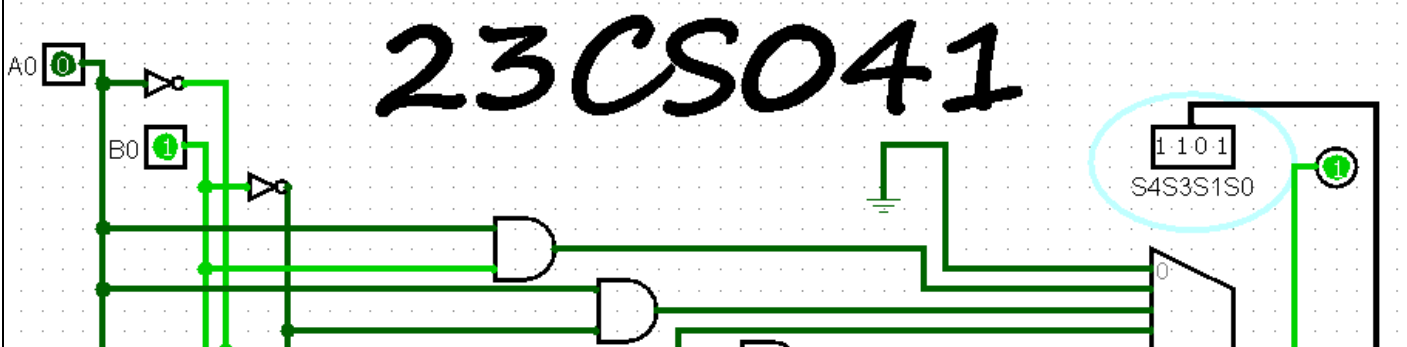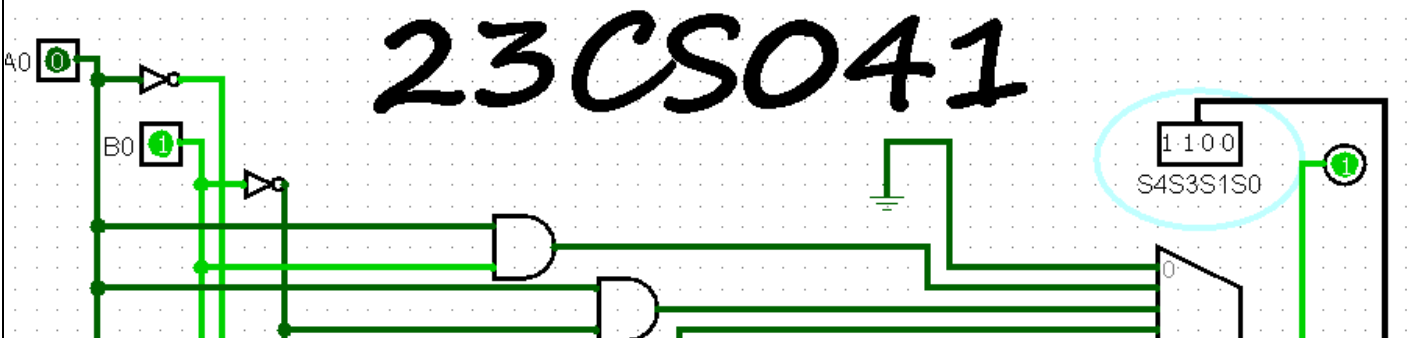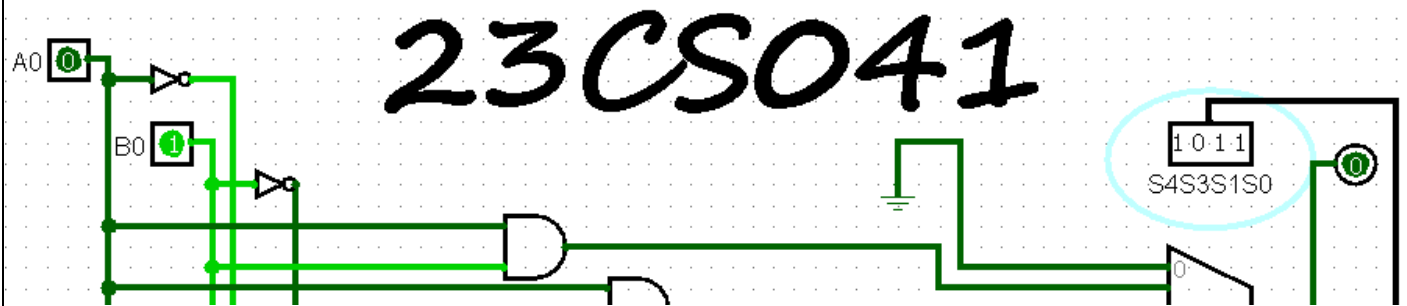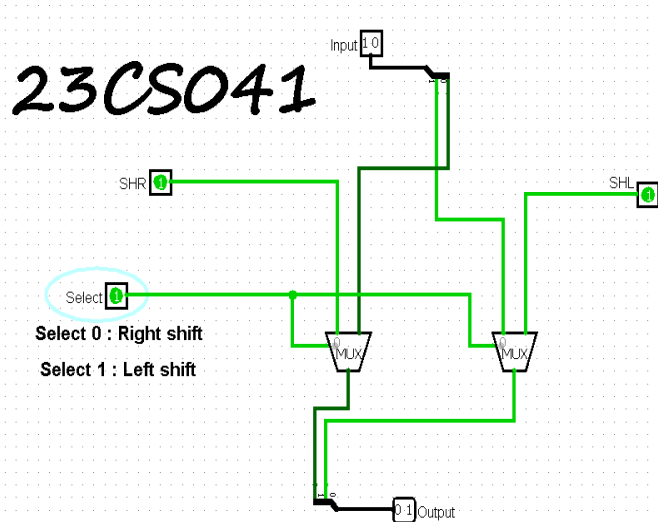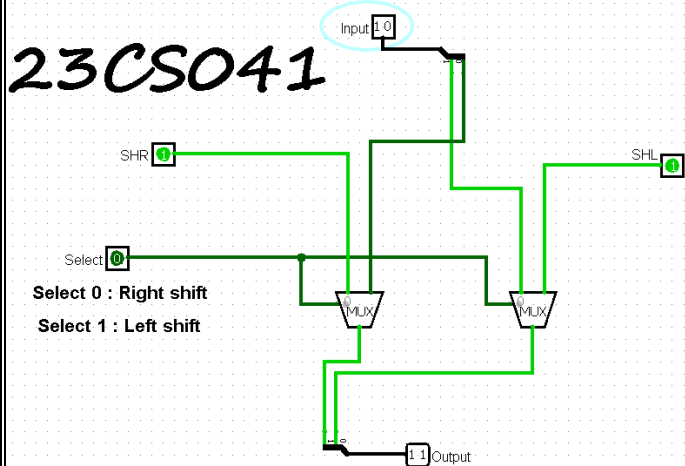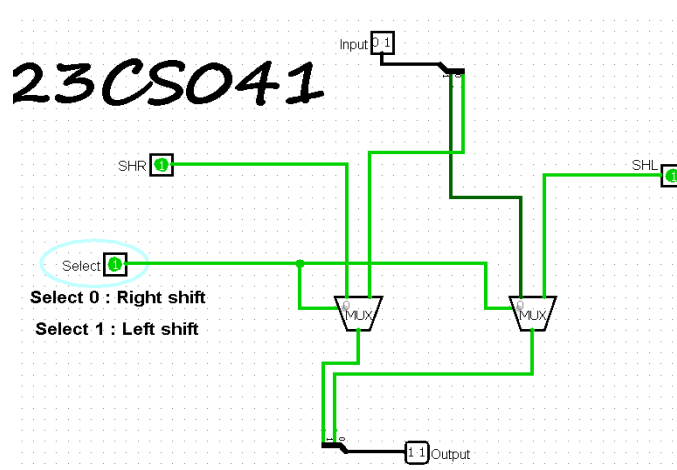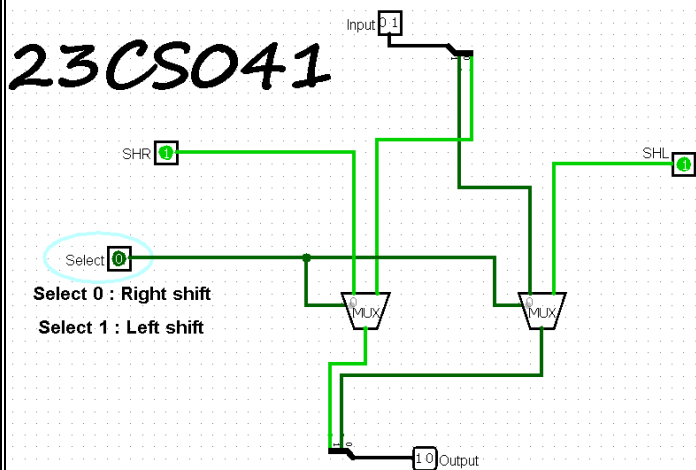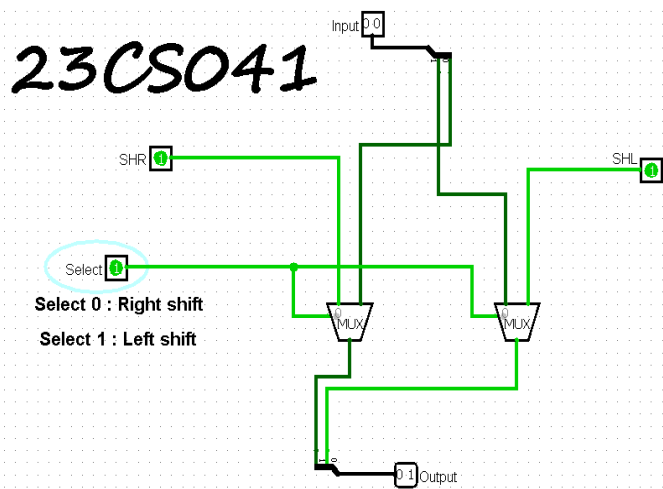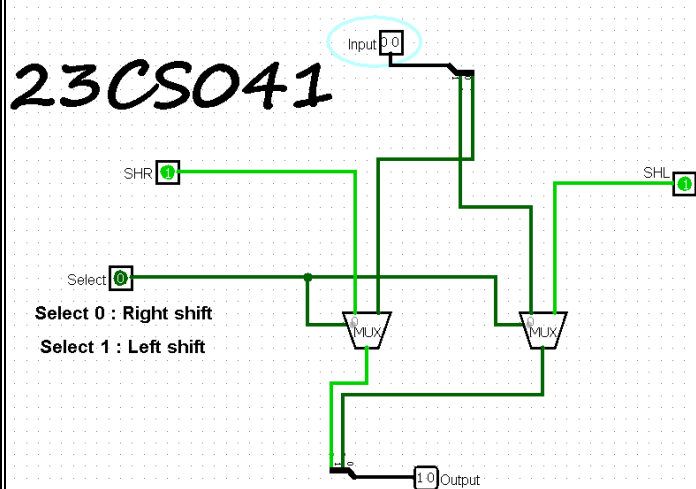


**iv. 1) 2-bit bidirectional shifter**

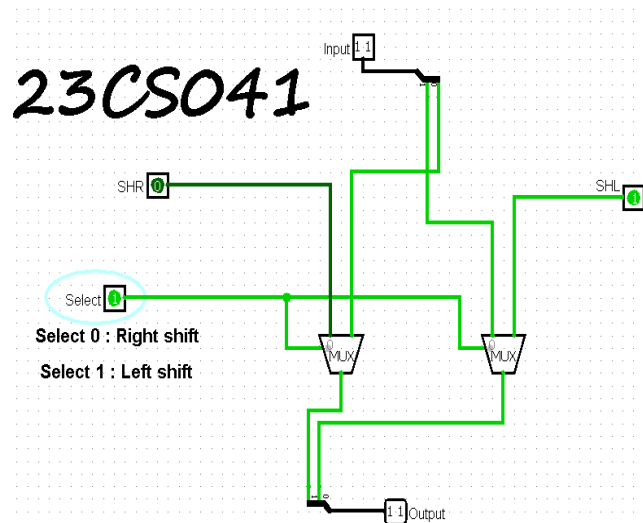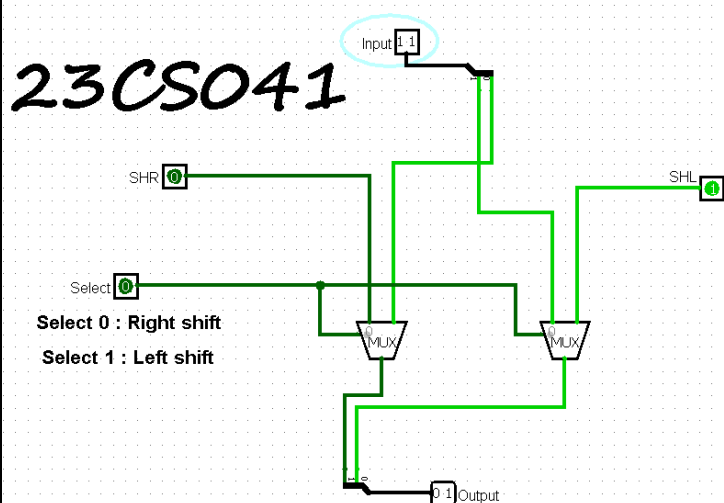


## 2) 4-bit bidirectional shifter

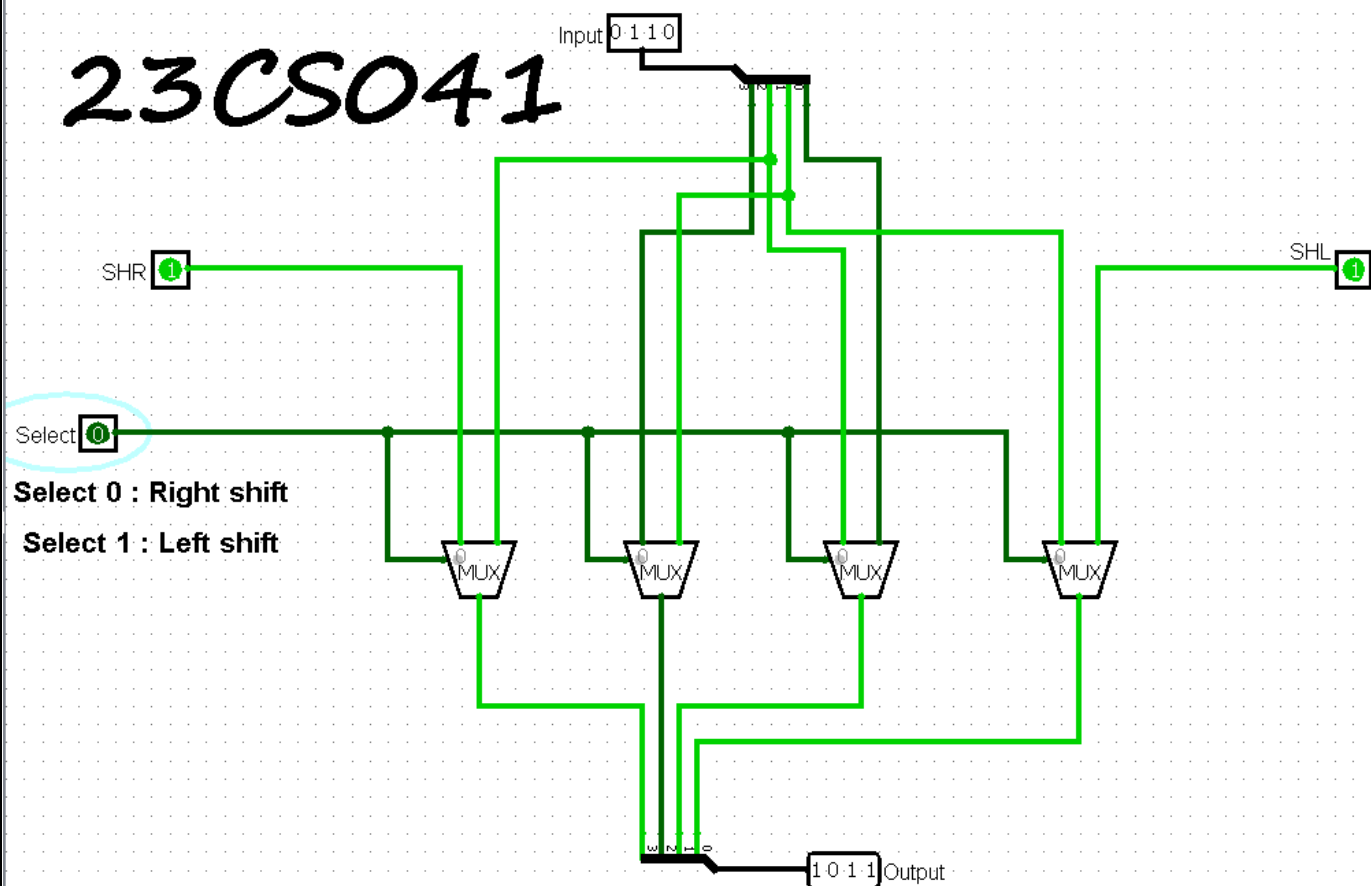


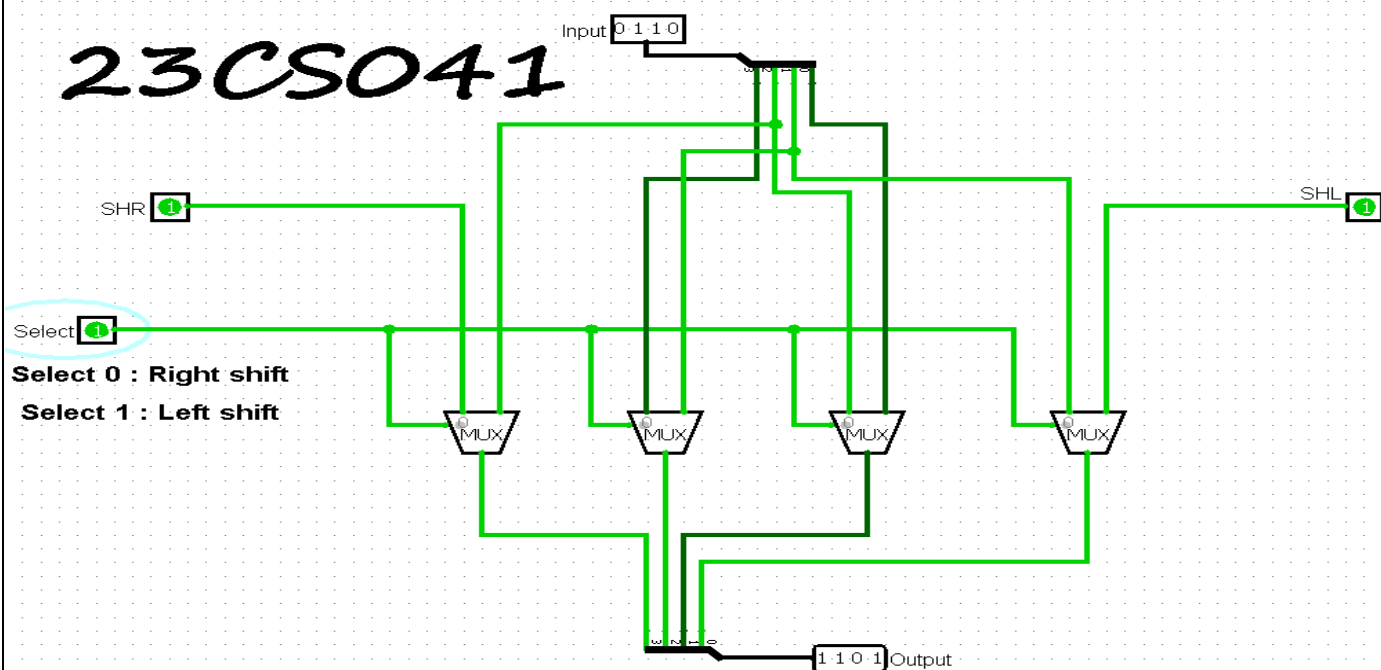





### 3) 8-bit bidirectional shifter






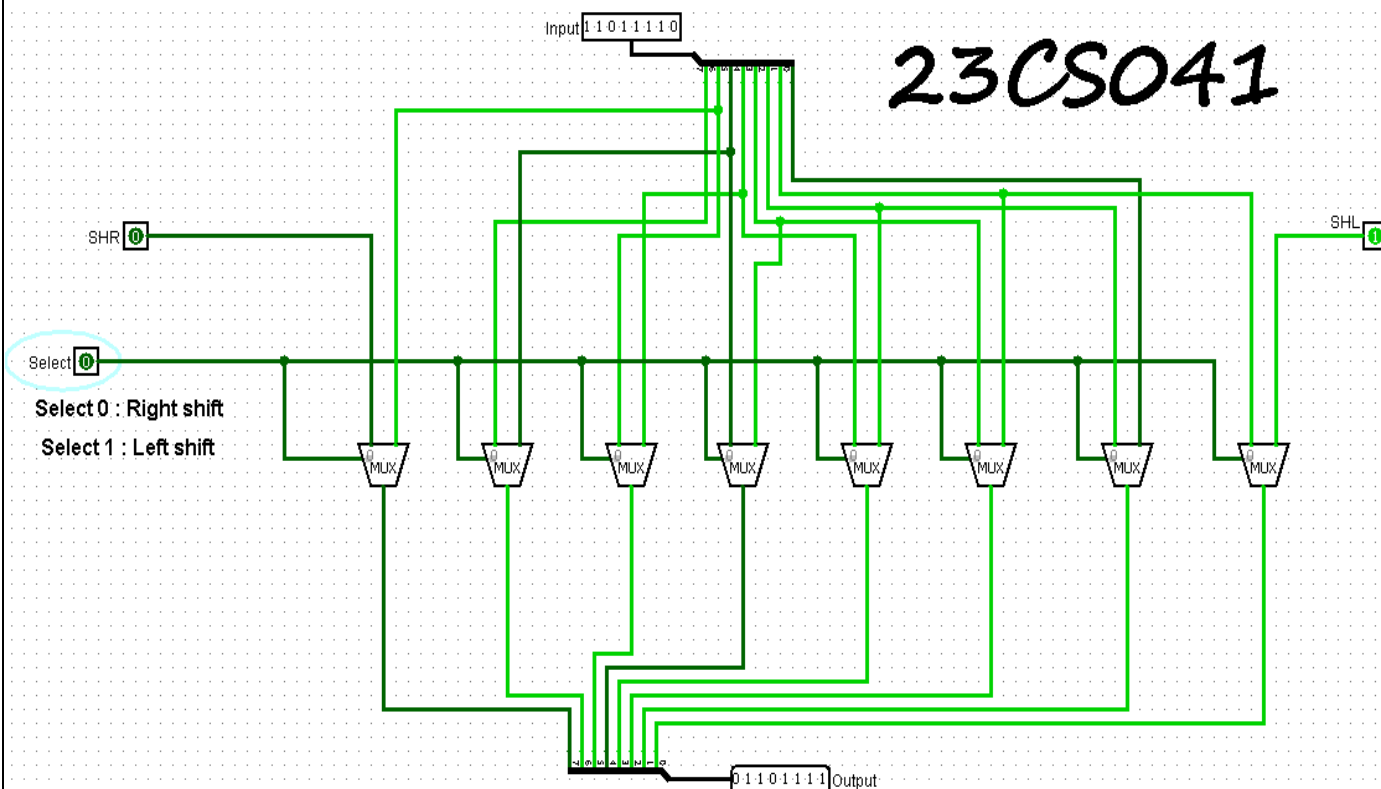




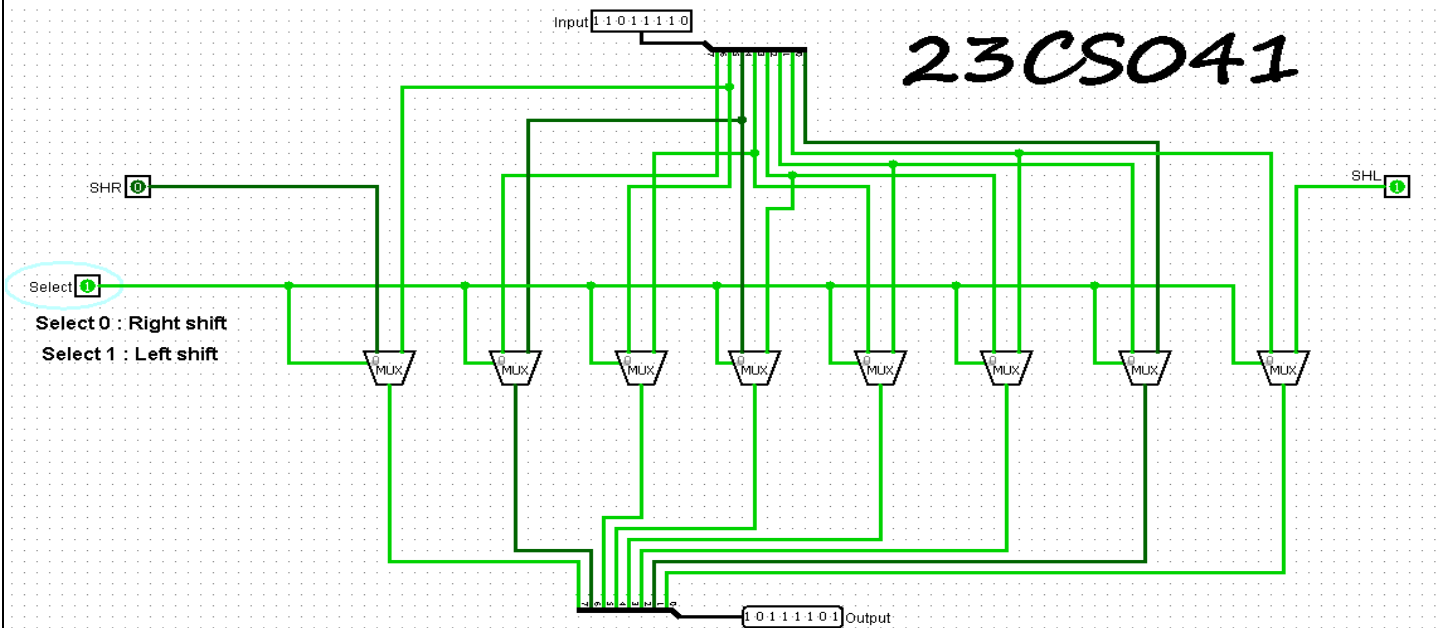



### v. 1) 1-bit ALU

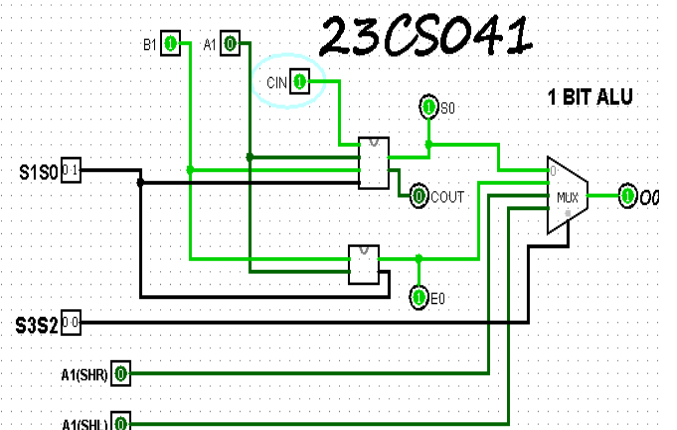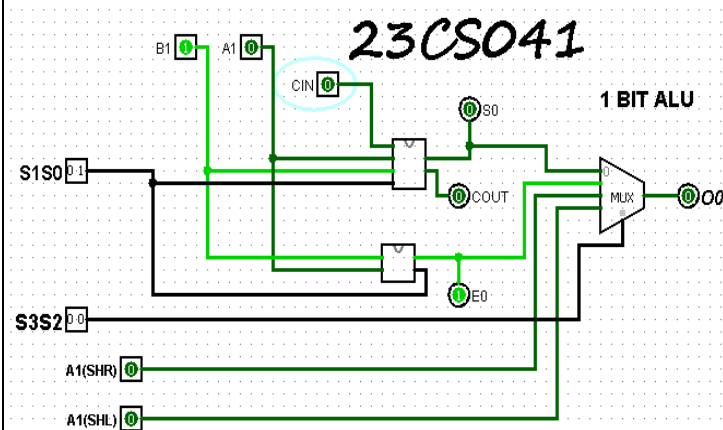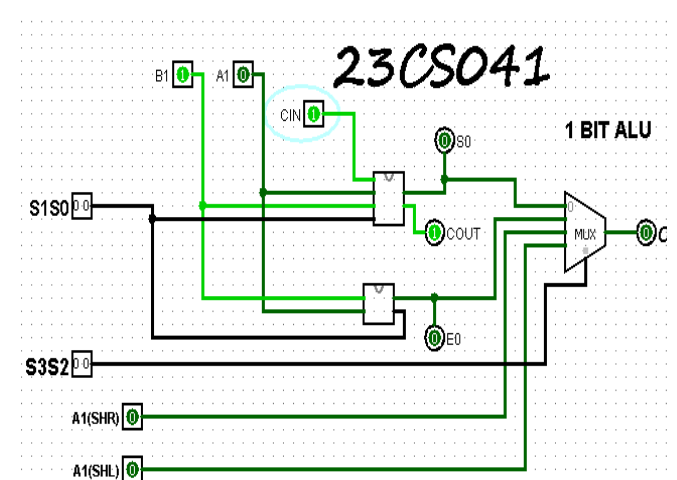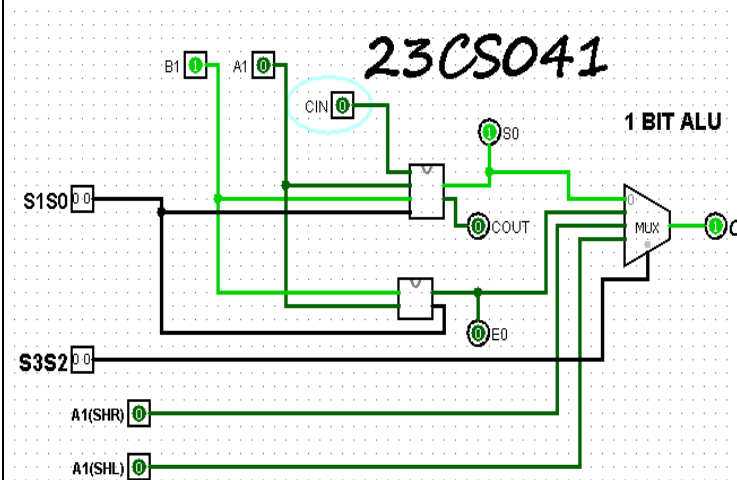


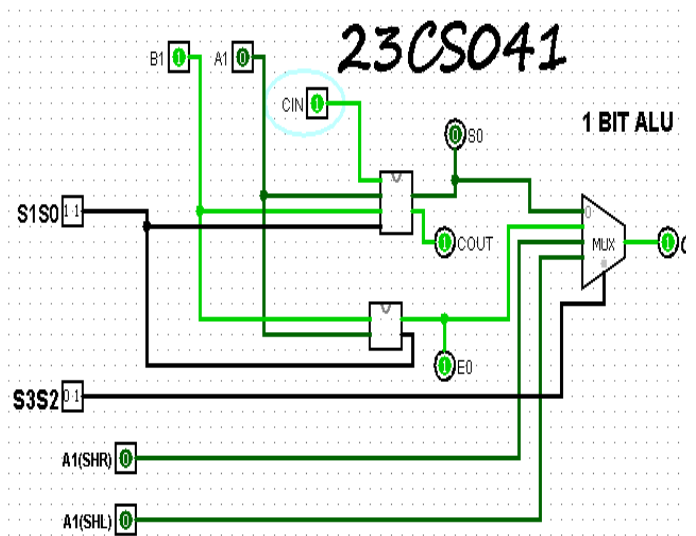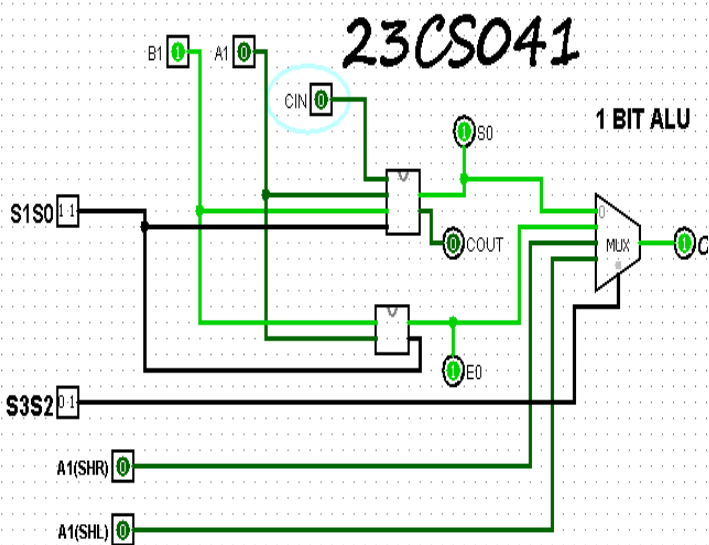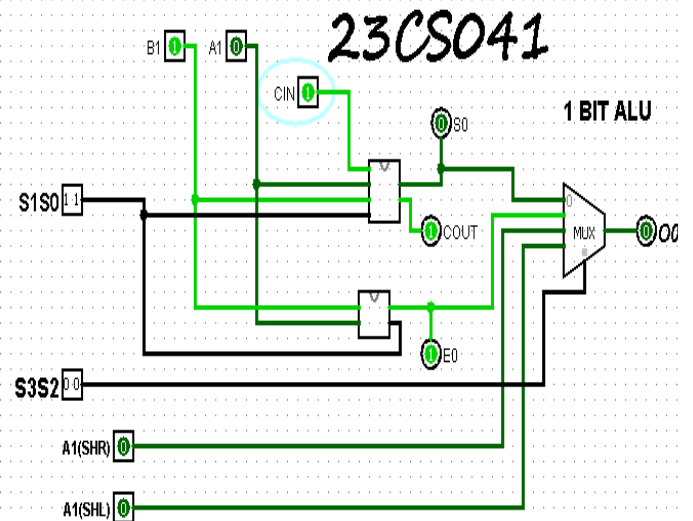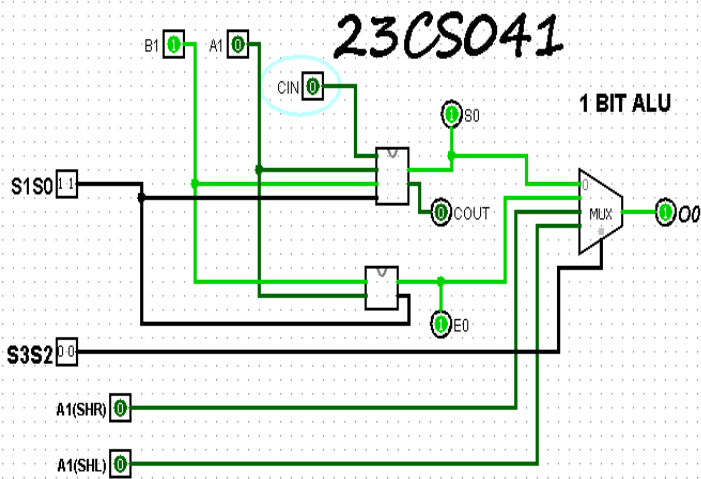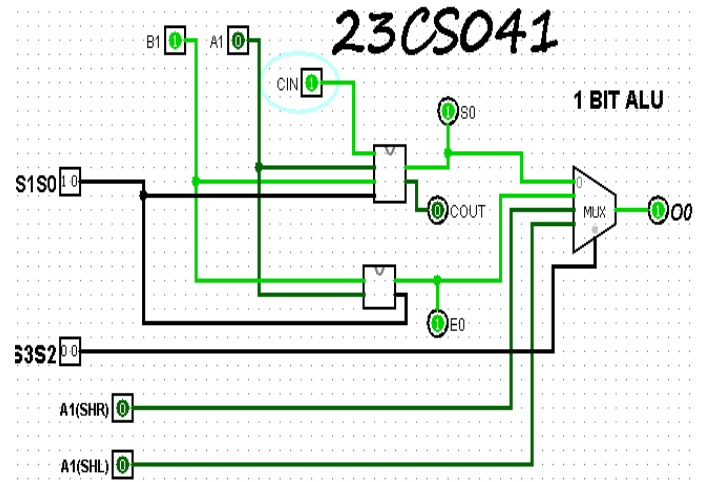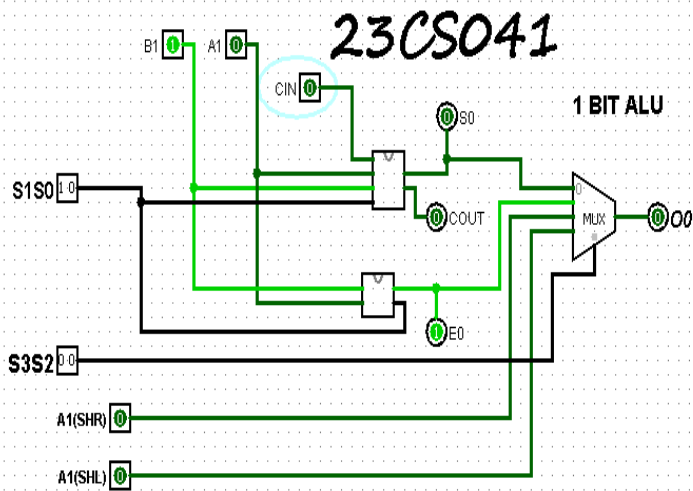

## 2) 4-bit ALU

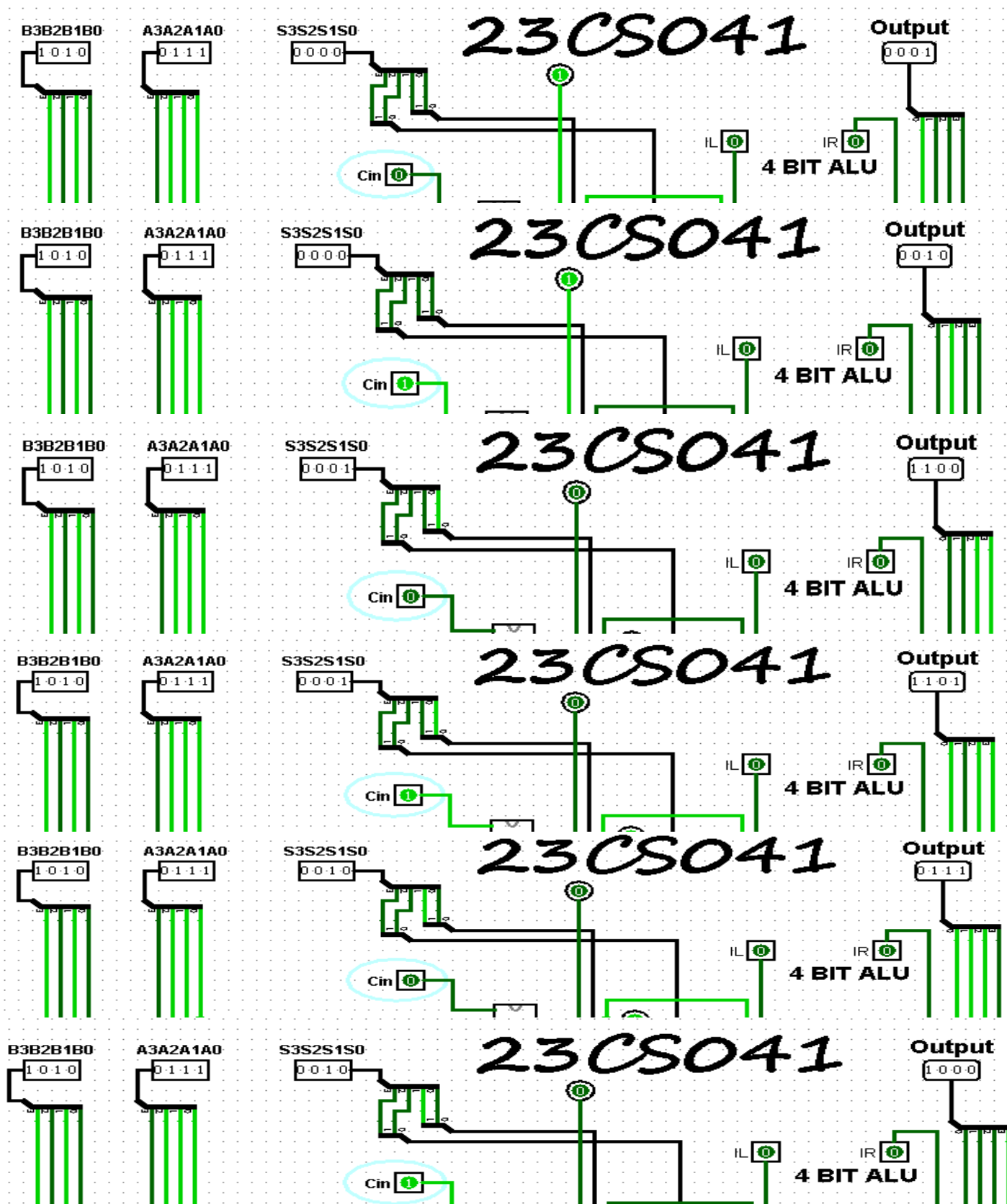

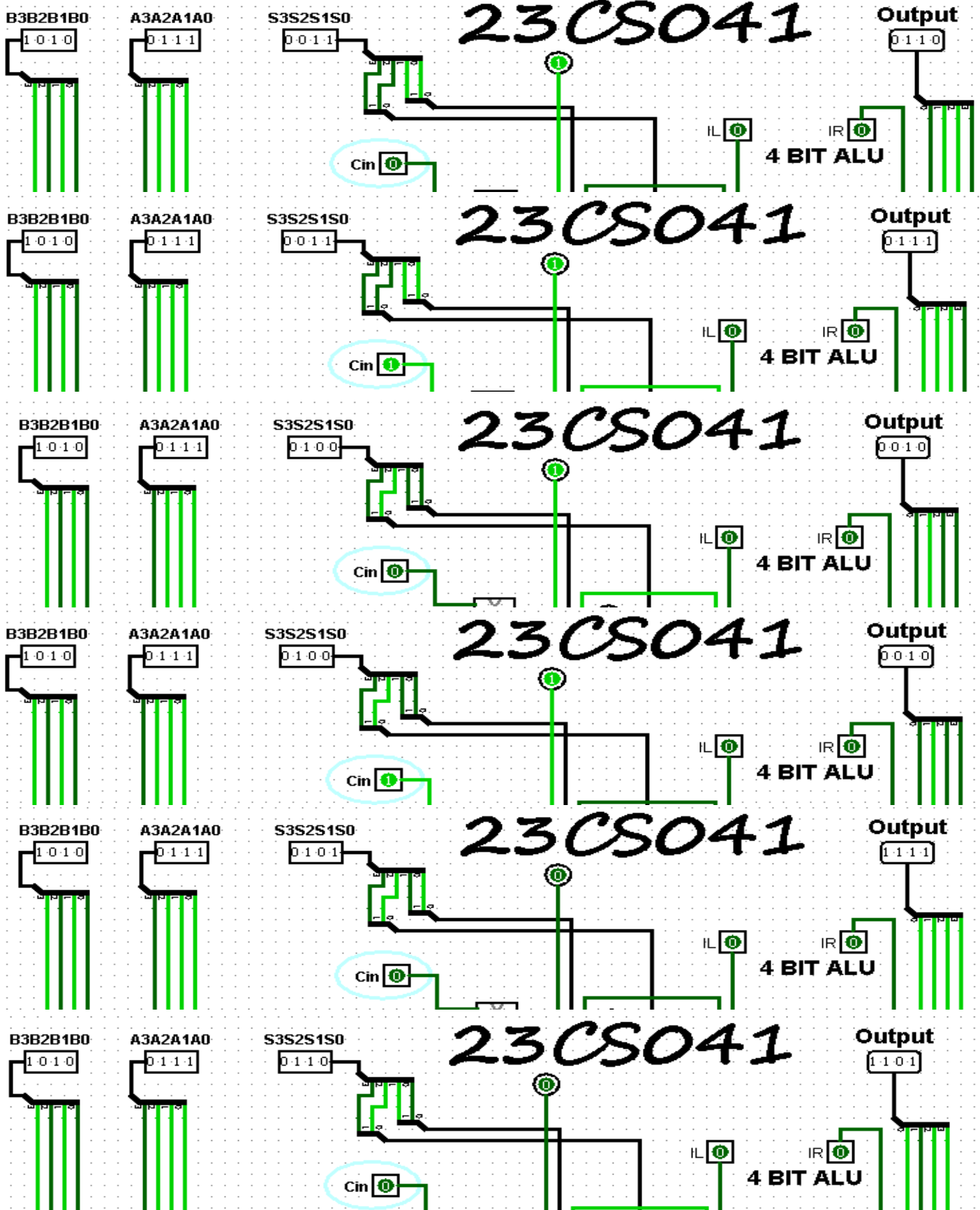

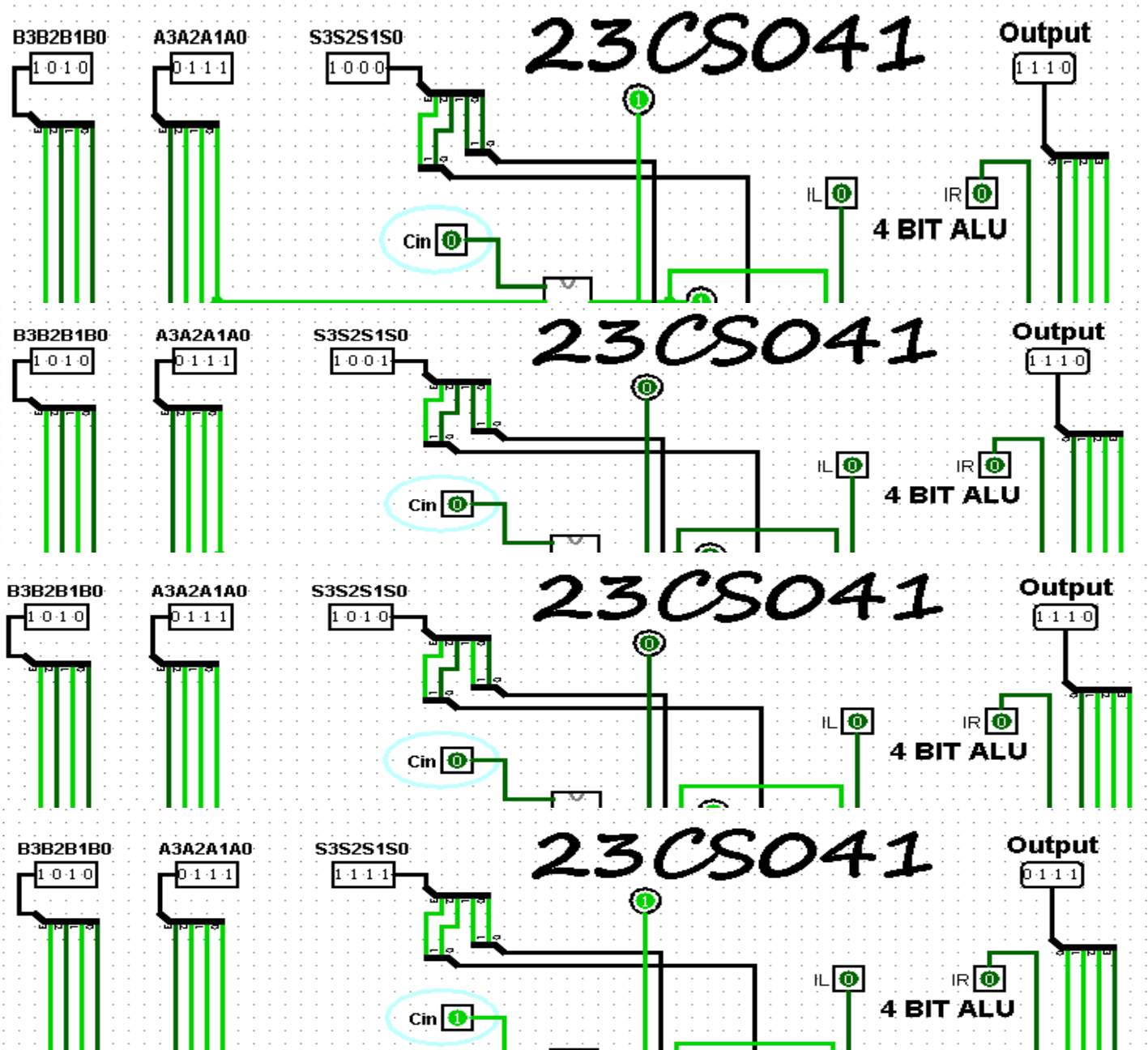

CONCLUSION: