


Date:

EXPERIMENT NO. 3


AIM: Implement a 4-bit common bus system to interface four 4-bit registers with a common bus using i. Multiplexer and ii. Decoder and tristate buffers.

CIRCUITS:

1) Multiplexer

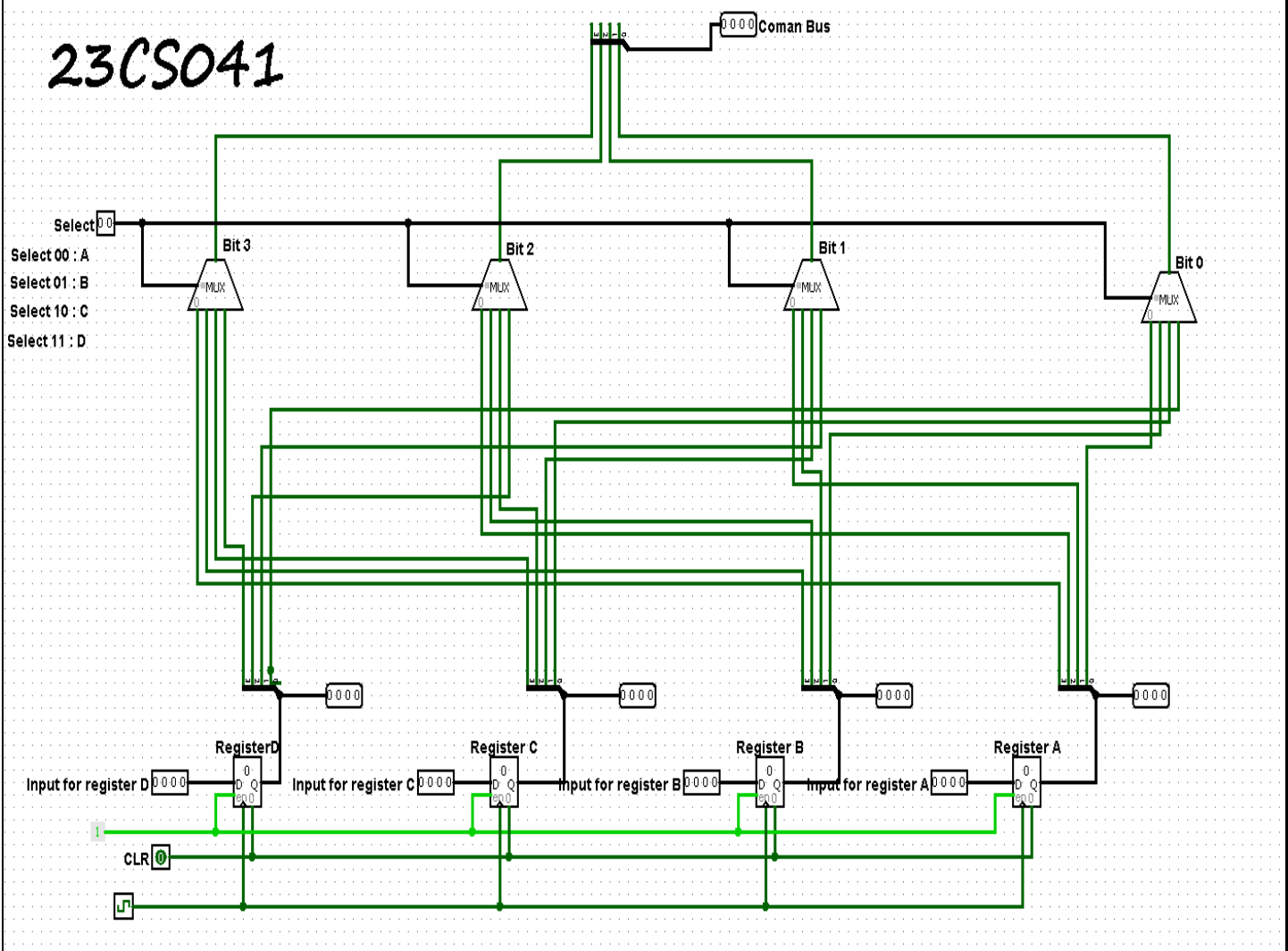


2) Decoder & tristate buffers

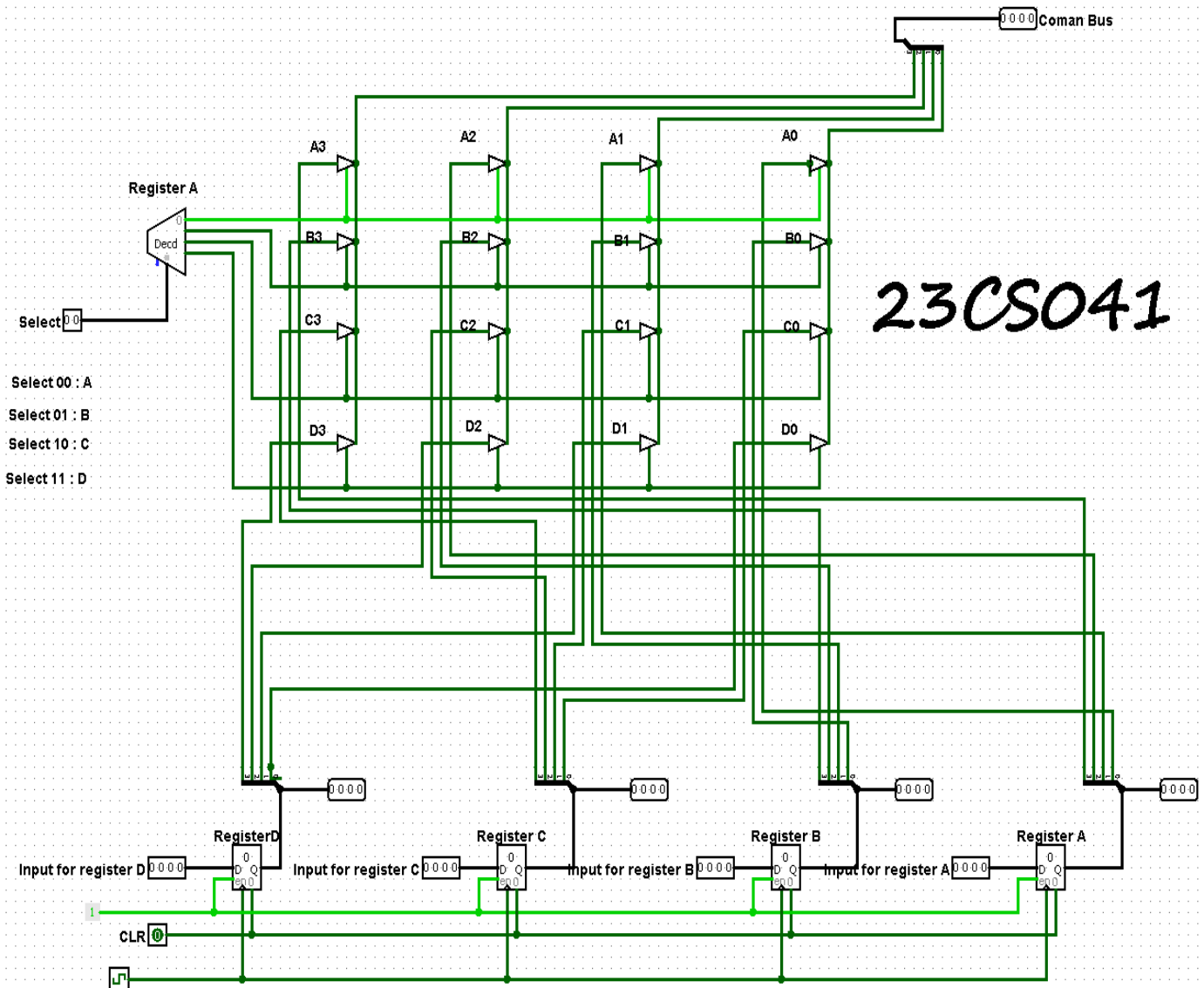


1)


23CS041

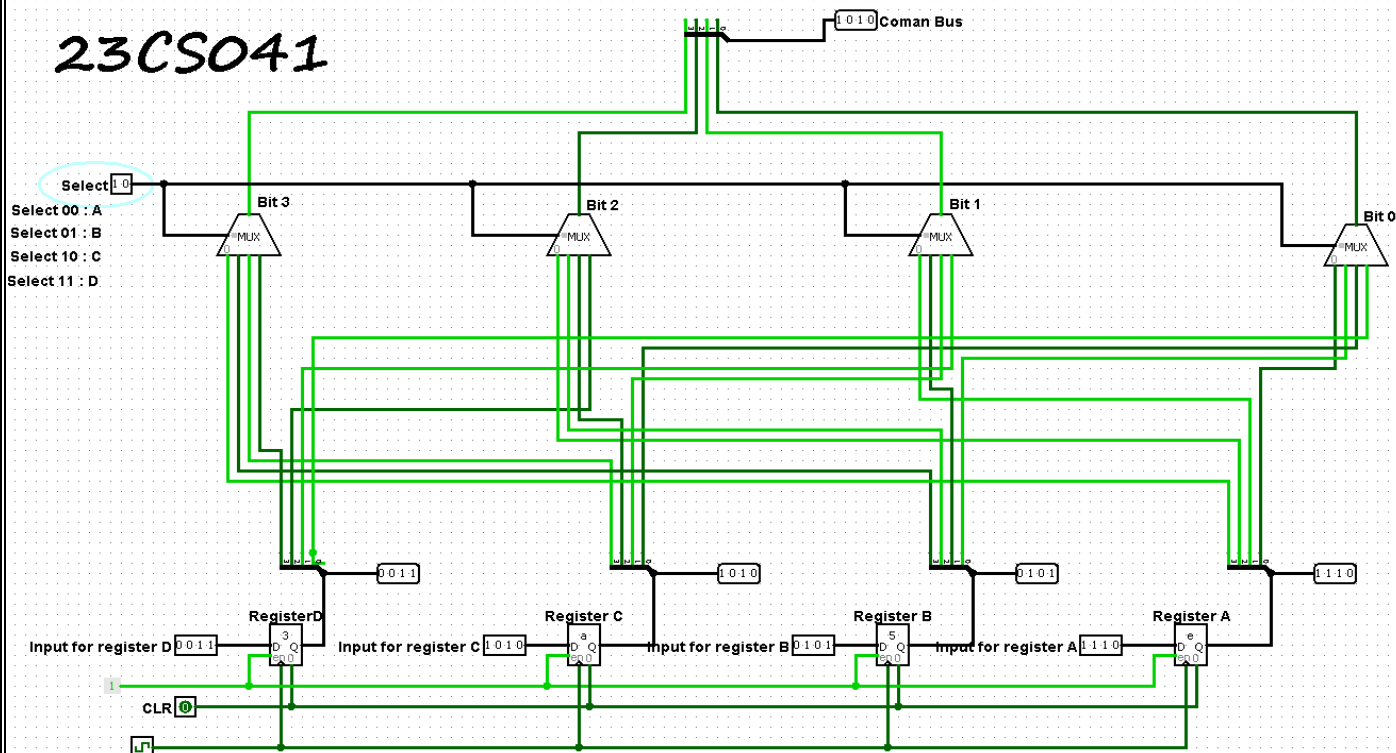


23CS041

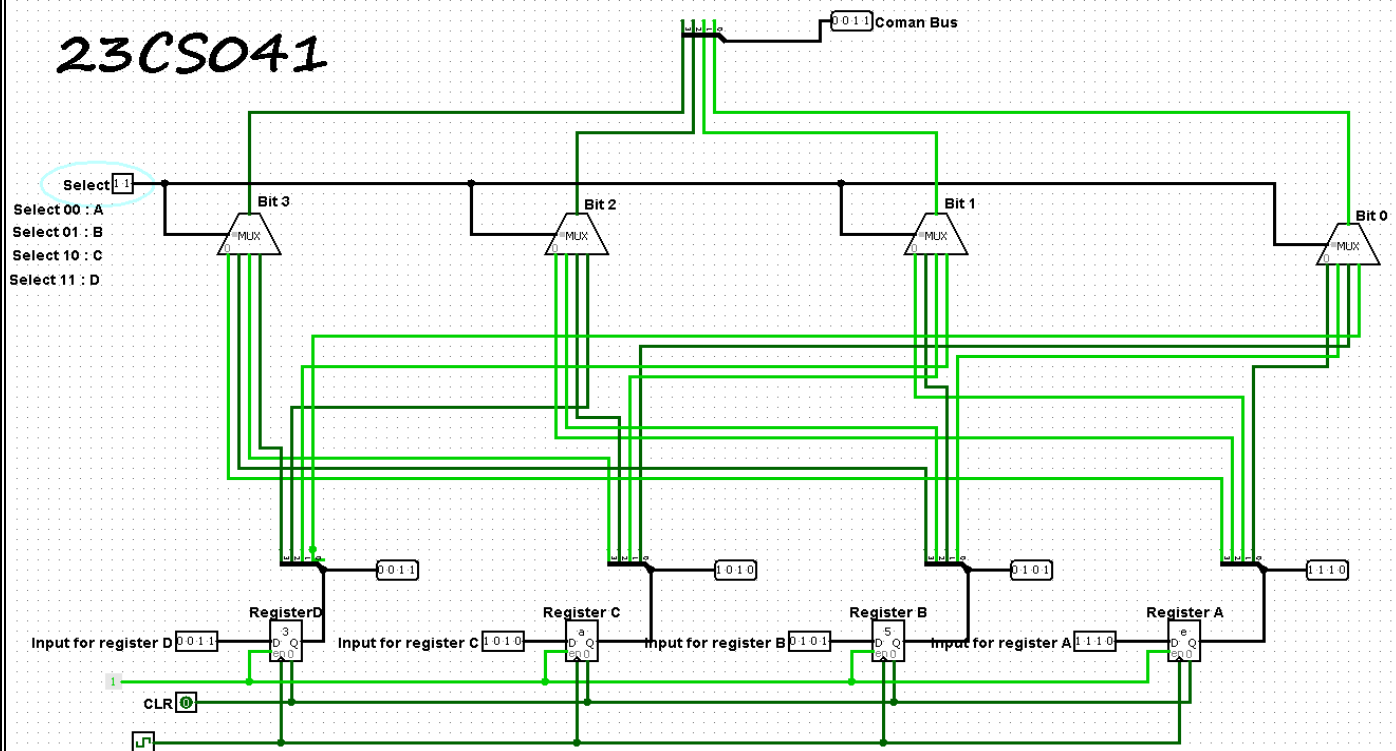

2)

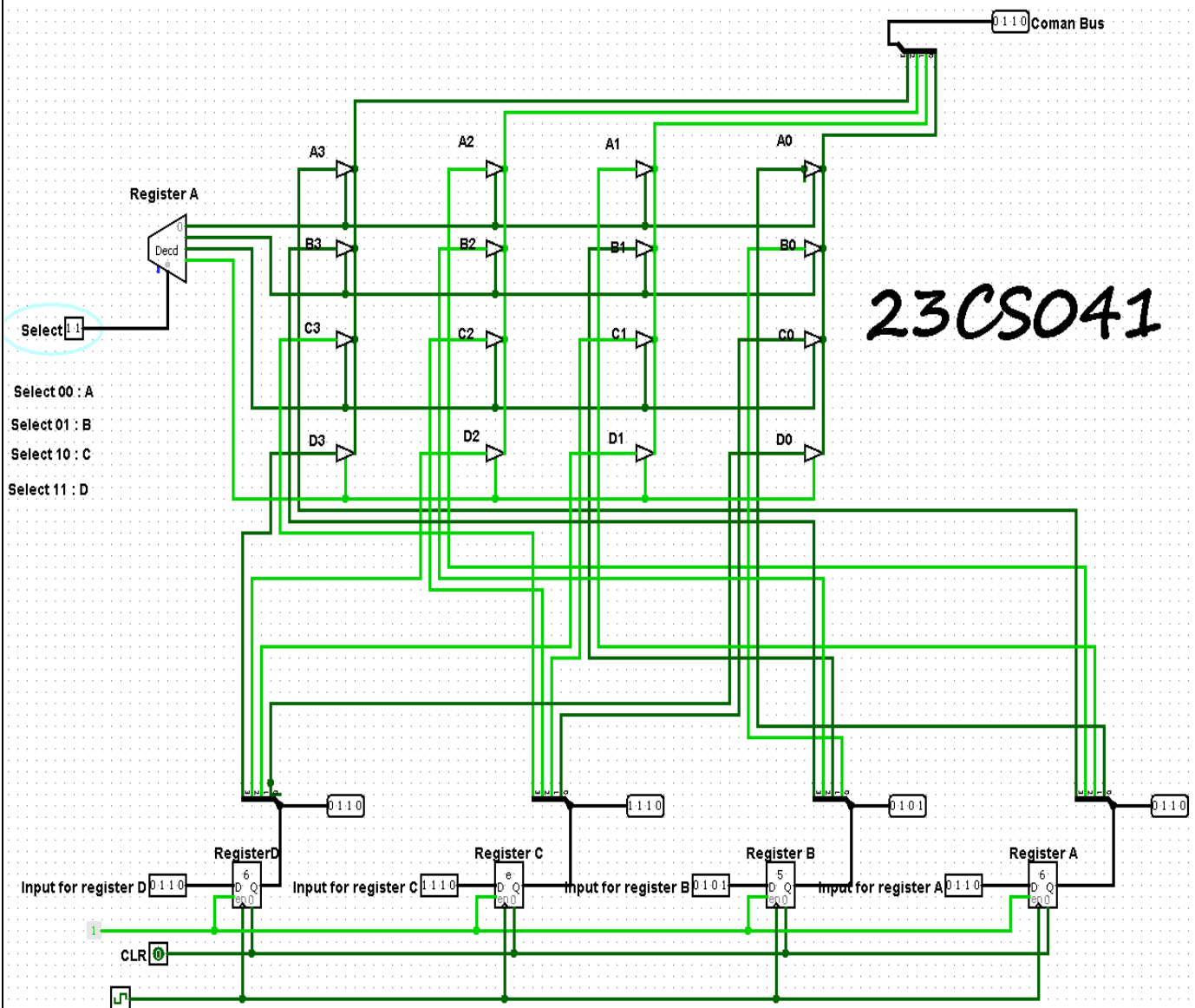

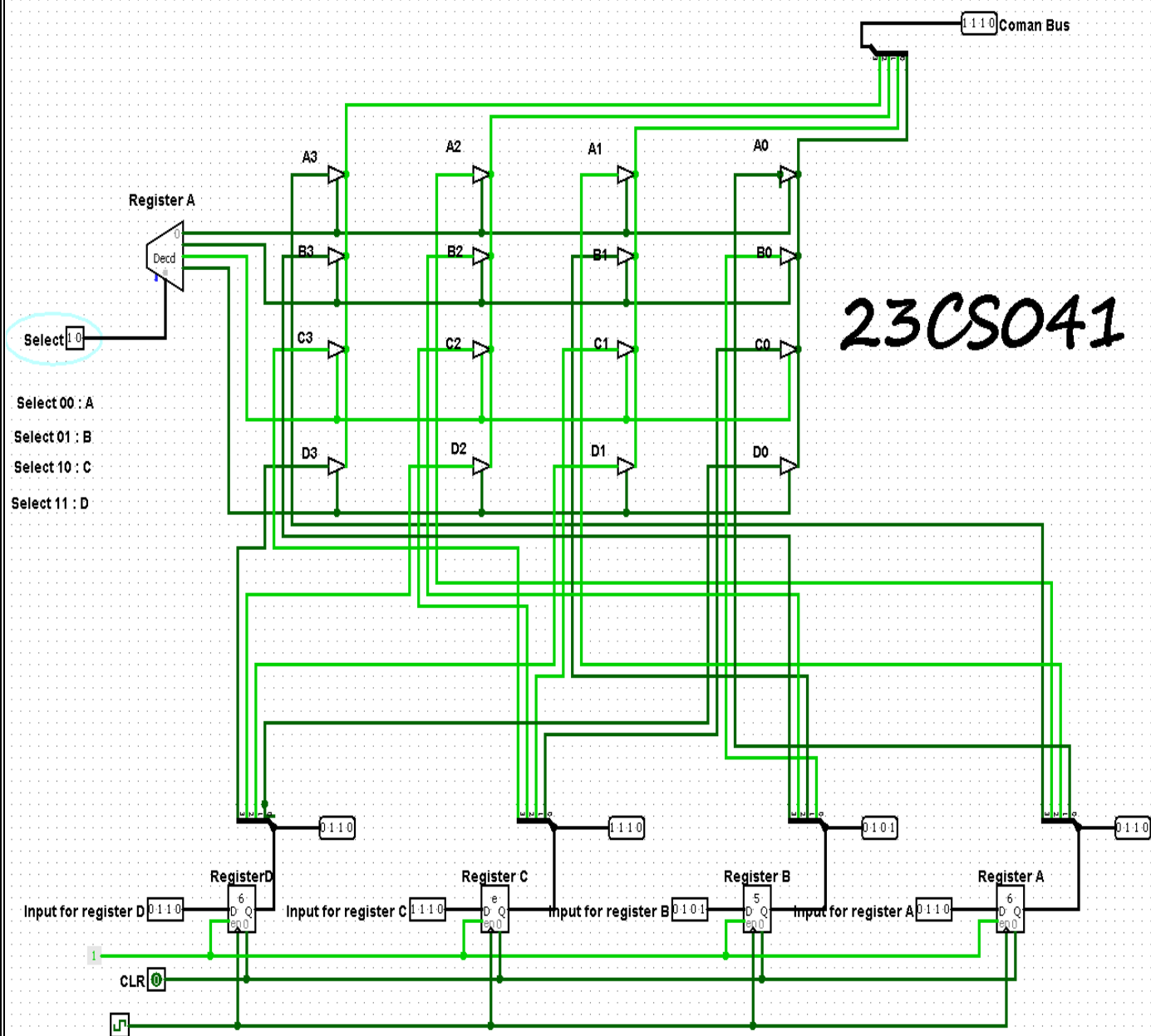

CONCLUSION:

POST SESSION EXERCISES:

1. Find a number $M = (\text{MOD}(\text{Last Three Digits of your enrolment number}, 5) + 3)$ and find a number $N = (\text{MOD}(\text{Last Three Digits of your enrolment number}, 3) + 3)$. Implement a M-bit common bus system to interface N M-bit registers with a common bus using i. Multiplexer and ii. Decoder and tristate buffers.

→ Last Three Digits of my enrolment number is 041.

$$\begin{aligned} M &= 41 \% 5 + 3 \\ &= 1 + 3 \\ M &= 4 \end{aligned}$$


$$\begin{aligned} N &= 41 \% 3 + 3 \\ N &= 2 + 3 \\ N &= 5 \end{aligned}$$

Number of Multiplexers: 4


Number of registers, $N = 5$

Since $N = 5$, we need a 3-to-8 decoder .
Number of Decoders = 1

we need $N \times M$ (5×4) tristate buffers.
A Number of Tristate Buffers = $N \times M = 5 \times 4 = 20$.

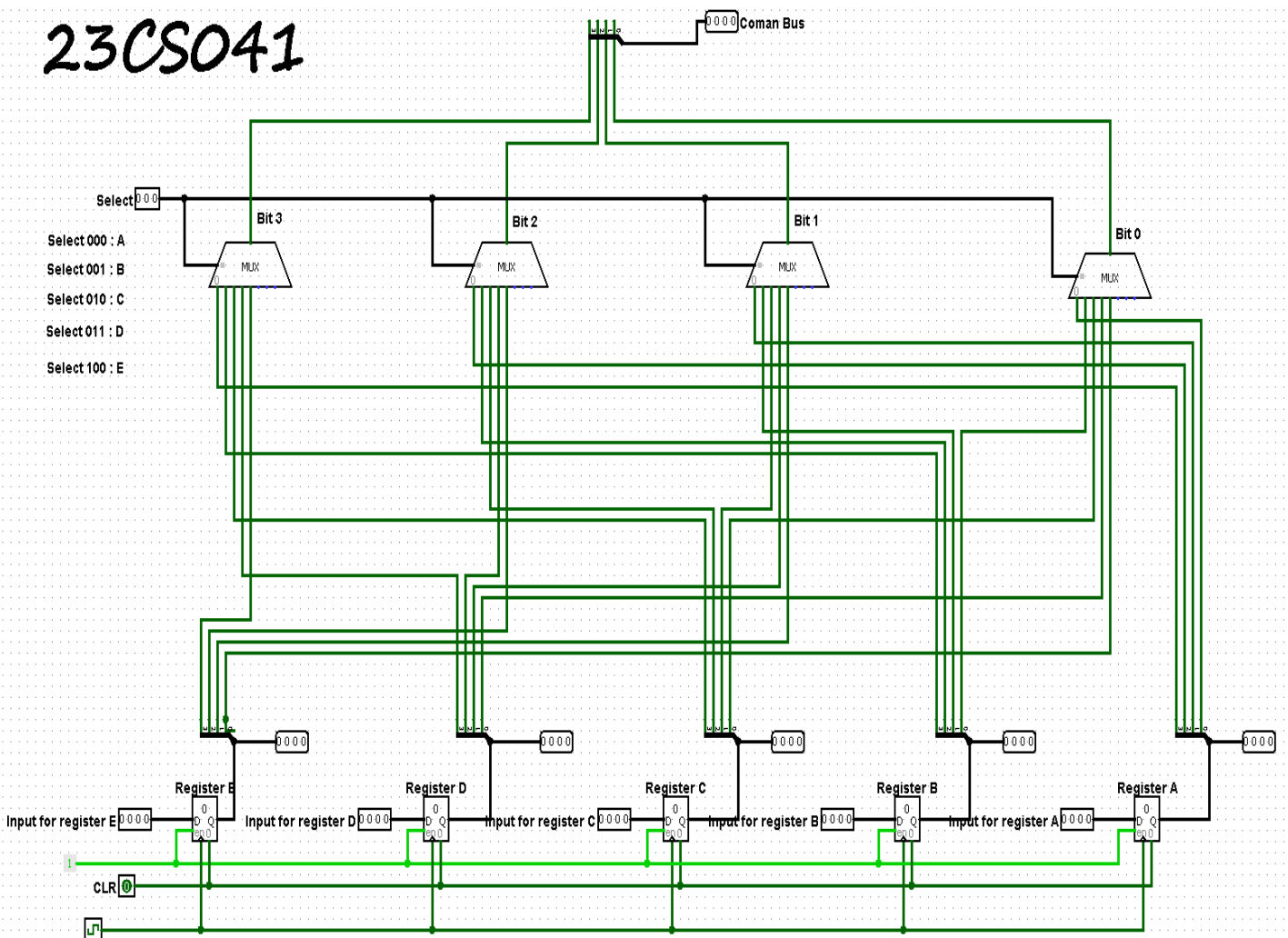
CIRCUITS:**1) Multiplexer**

2) Decoder & tristate buffers

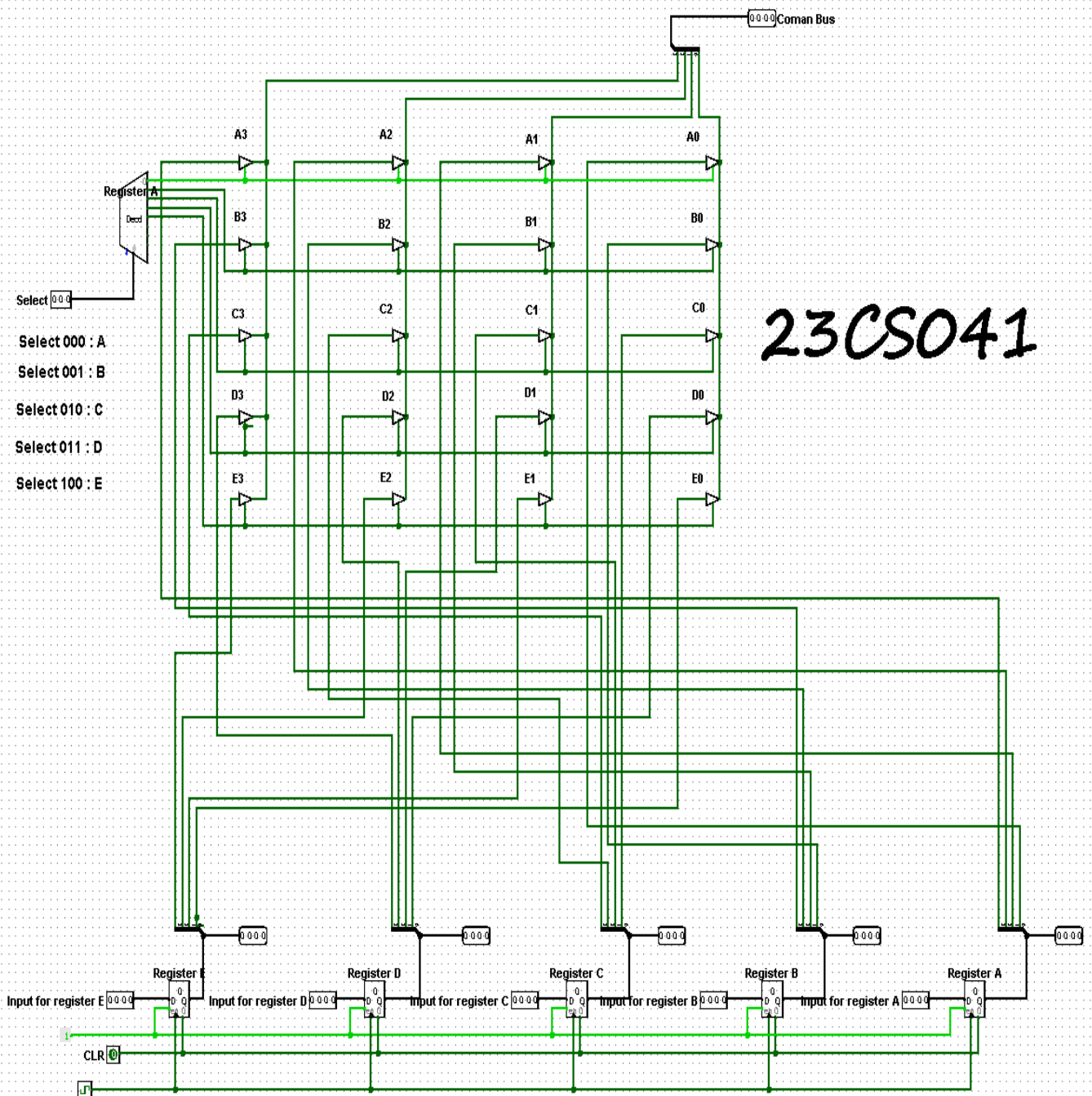


1)

23CS041

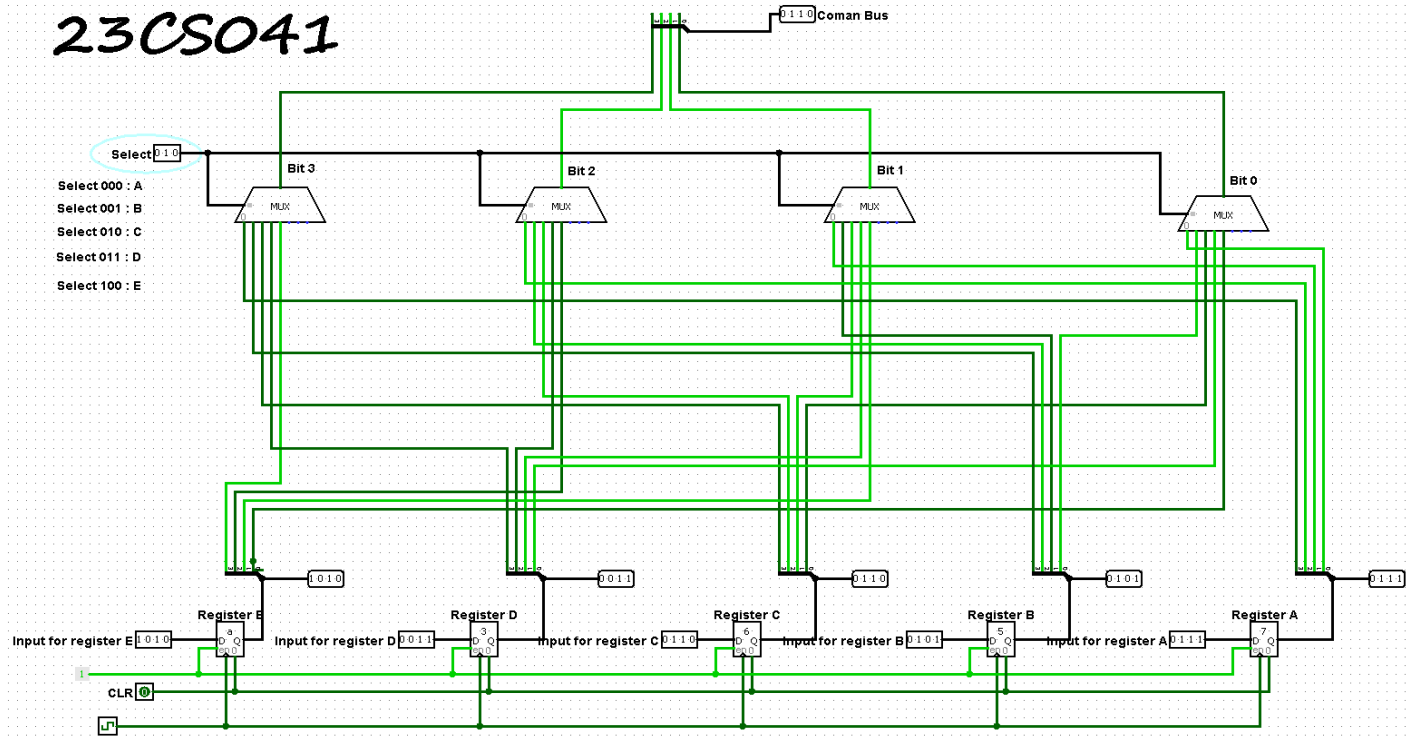

23CS041

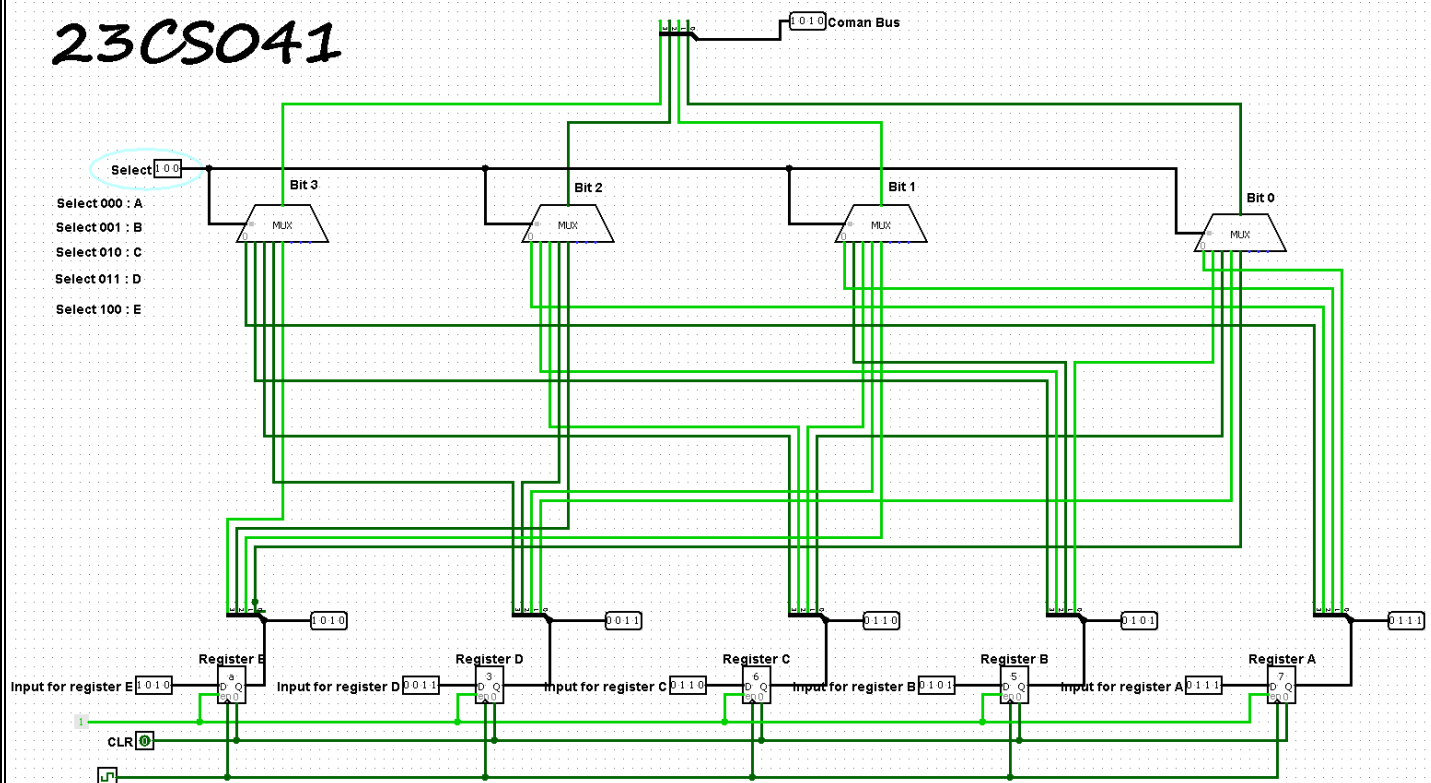

2)

